

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

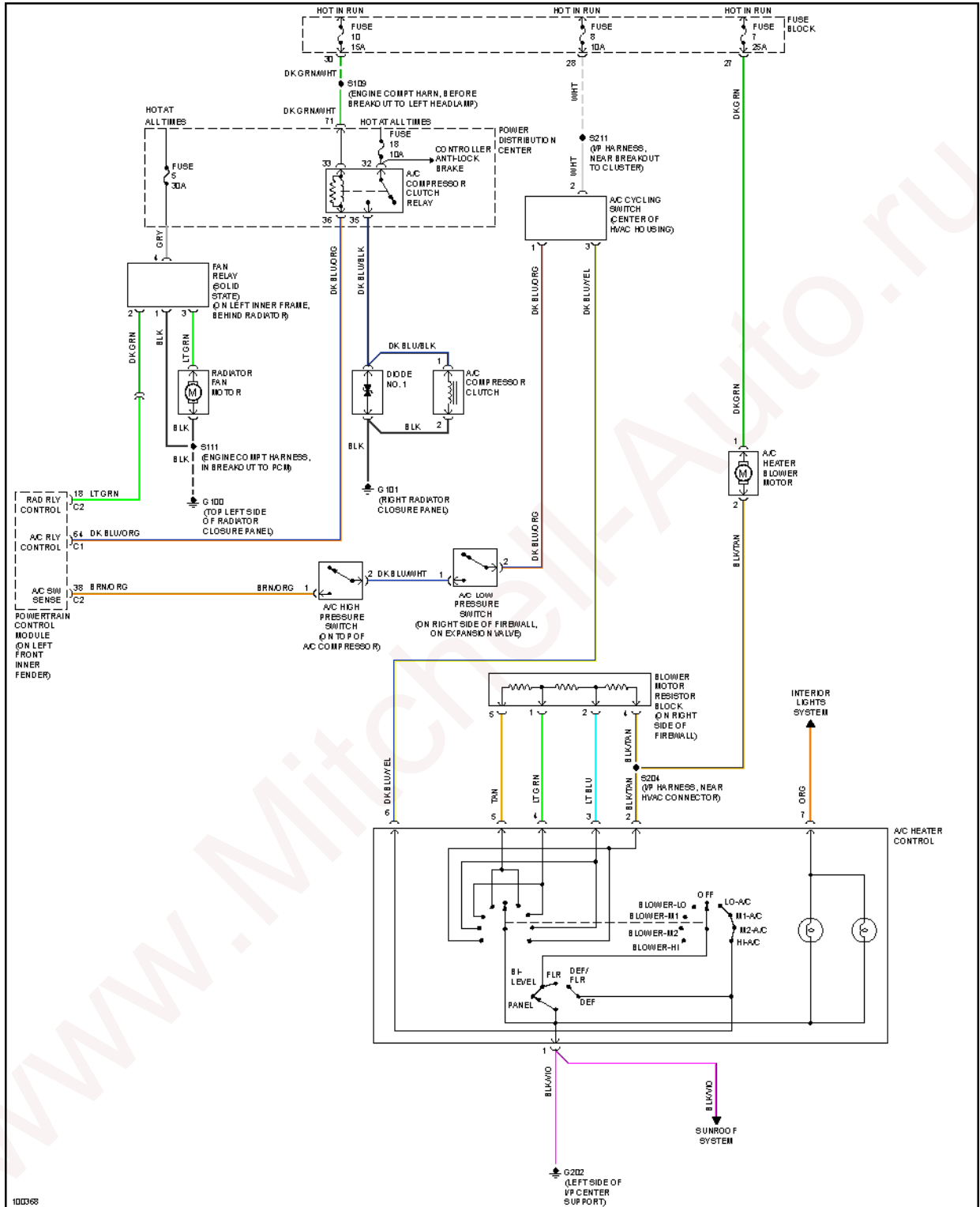


Fig. 1: A/C Circuit

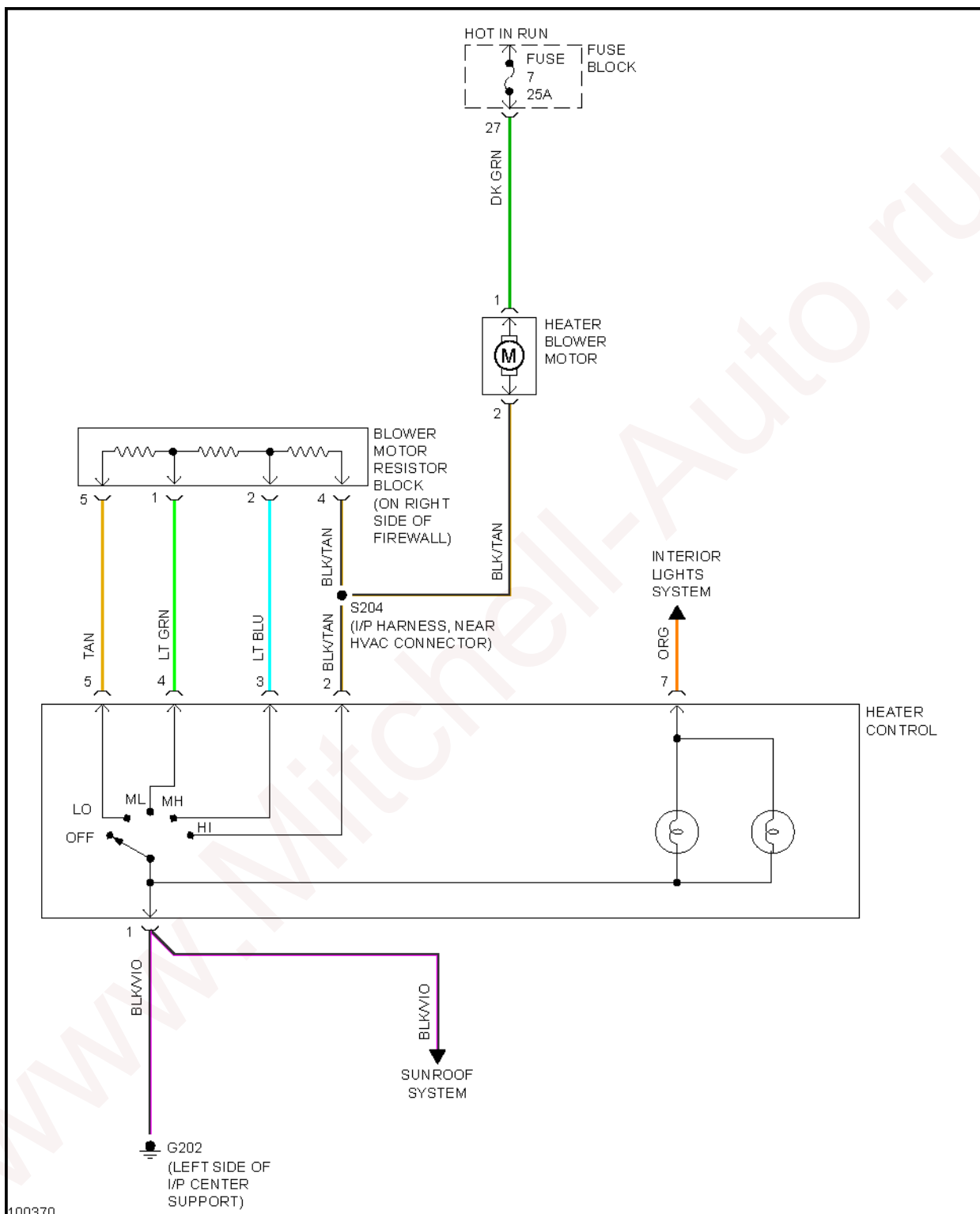


Fig. 2: Heater Circuit

ANTI-LOCK BRAKES

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

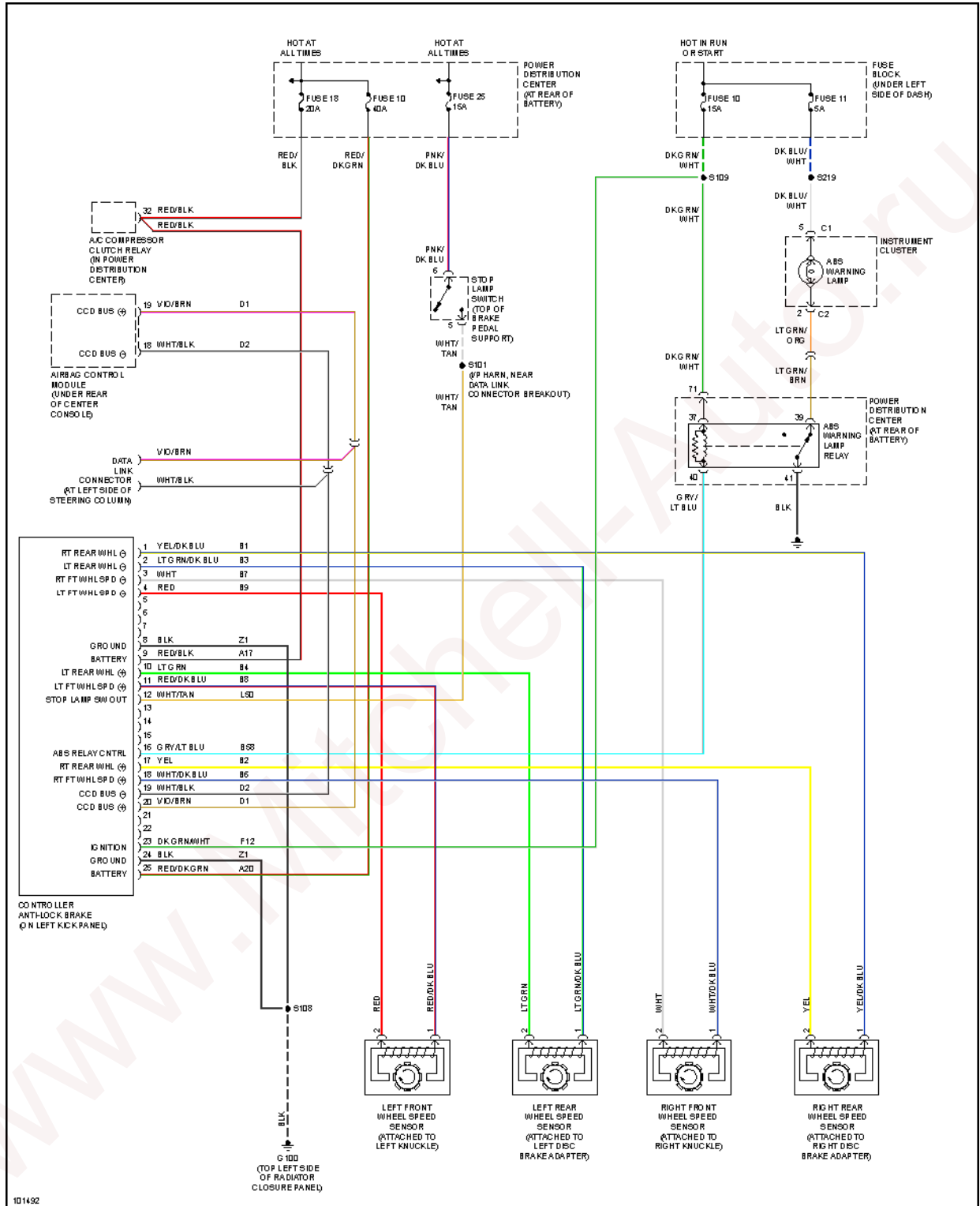


Fig. 3: Anti-lock Brake Circuits

COMPUTER DATA LINES

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

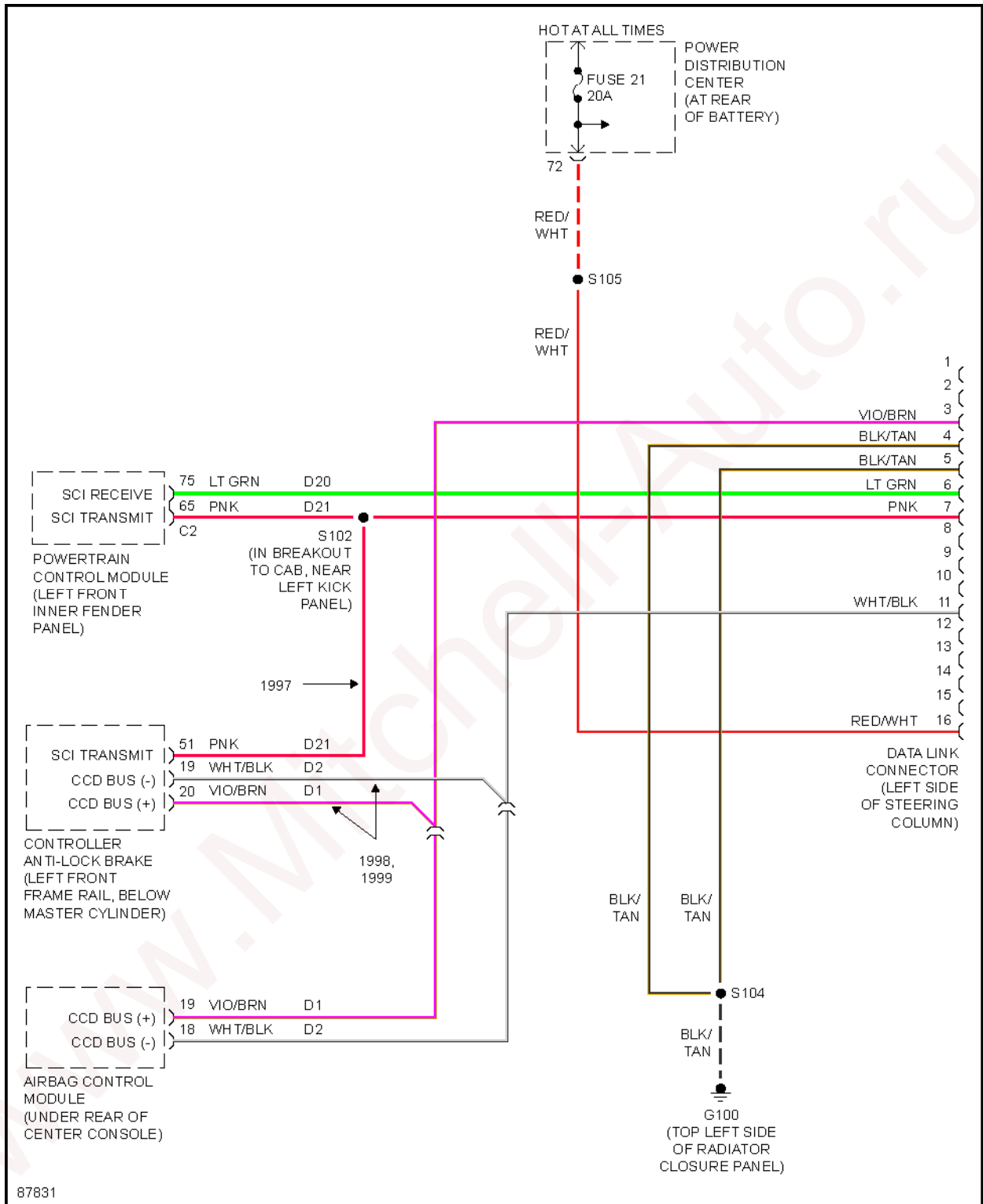


Fig. 4: Computer Data Lines

COOLING FAN

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

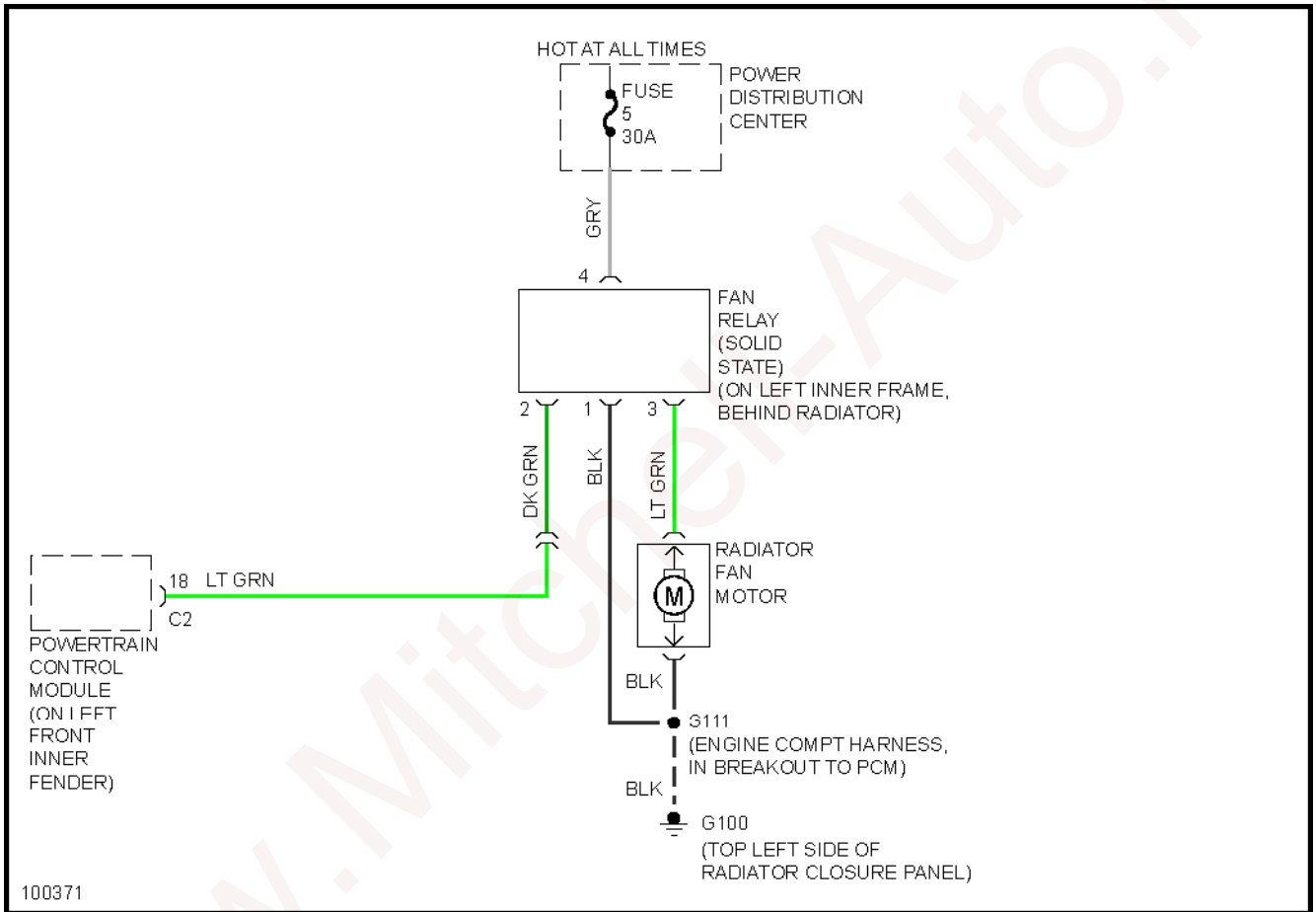


Fig. 5: Cooling Fan Circuit

CRUISE CONTROL

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

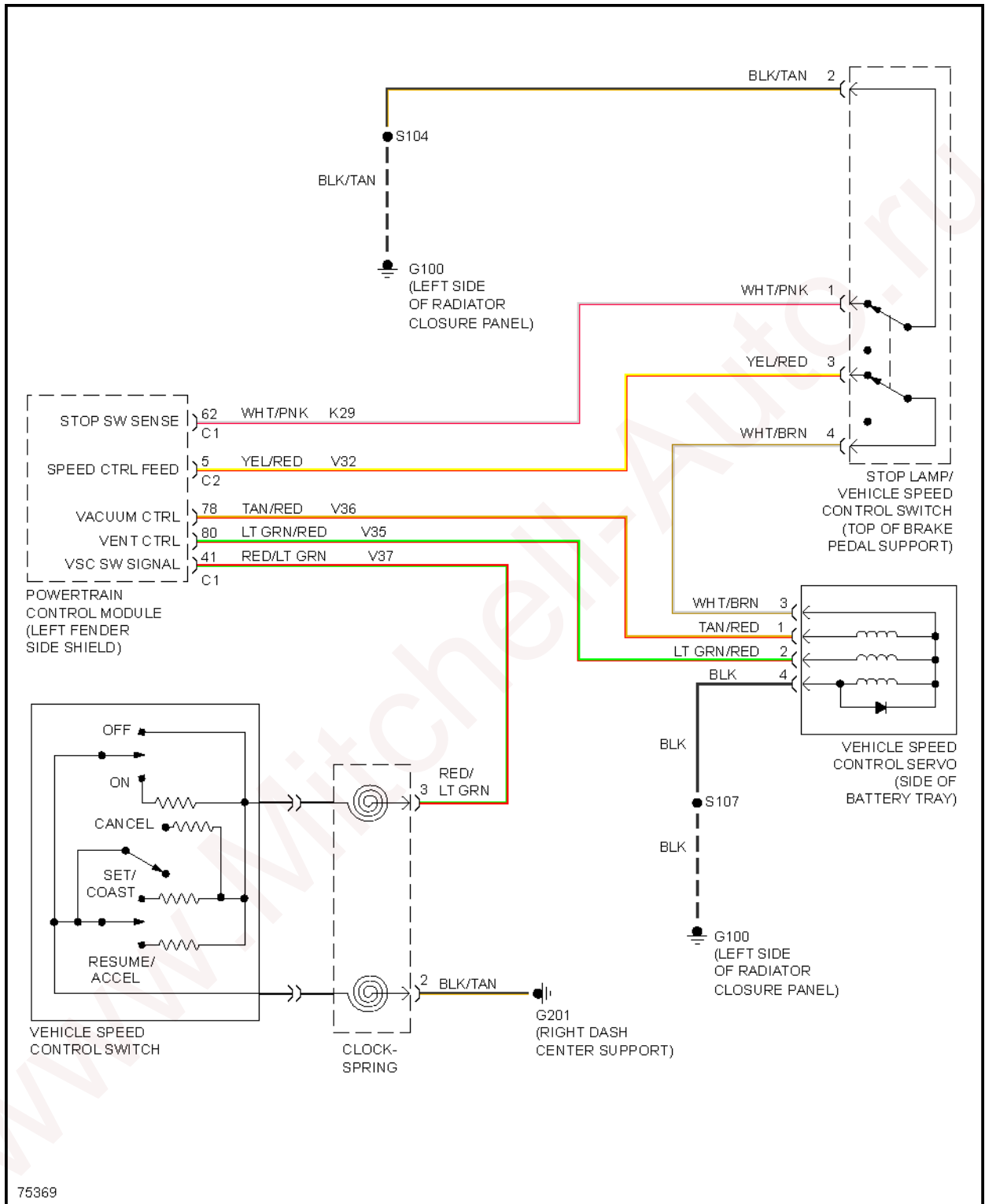


Fig. 6: Cruise Control Circuit

DEFOGGERS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

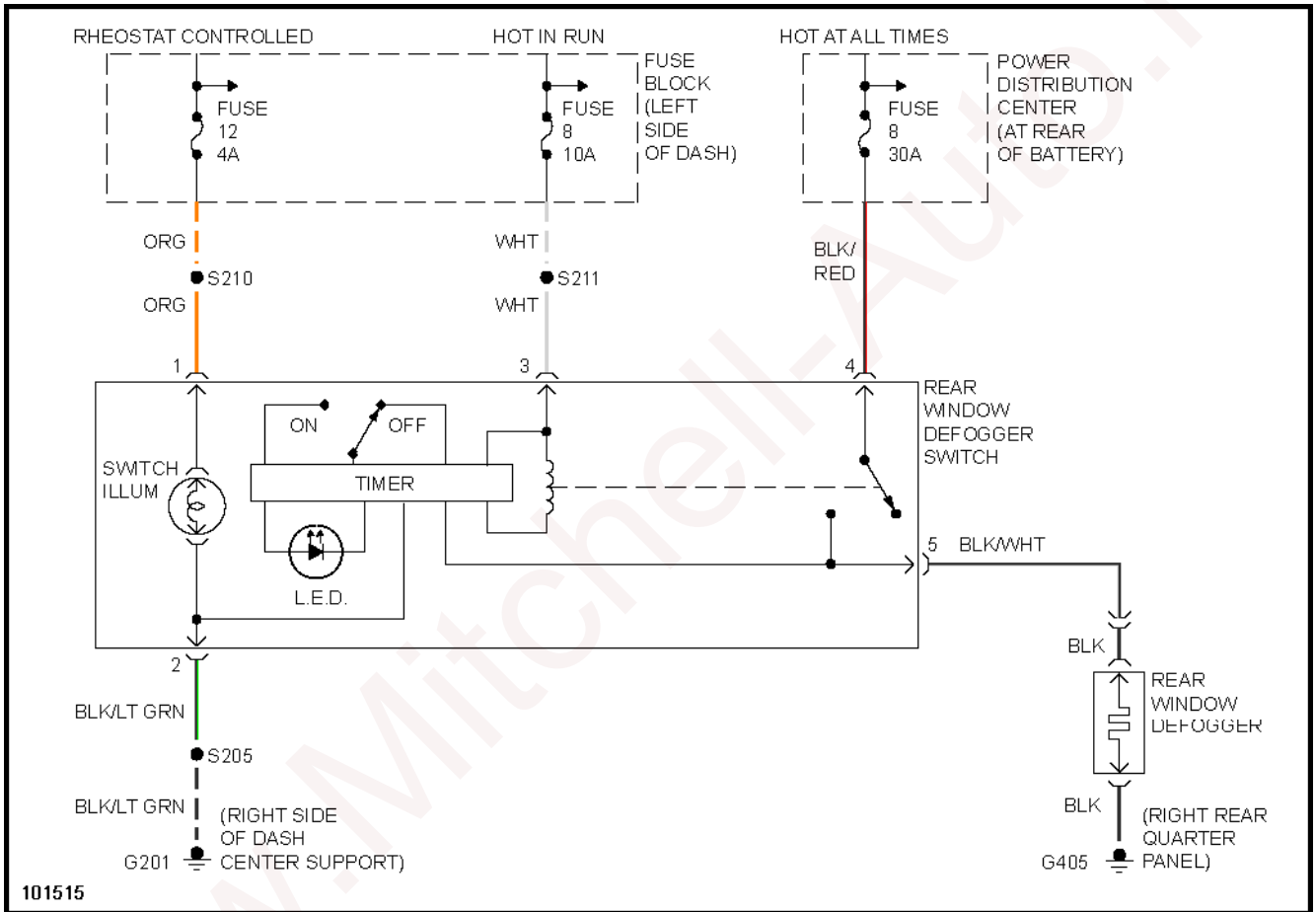


Fig. 7: Defogger Circuit

ENGINE PERFORMANCE

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

2.0L

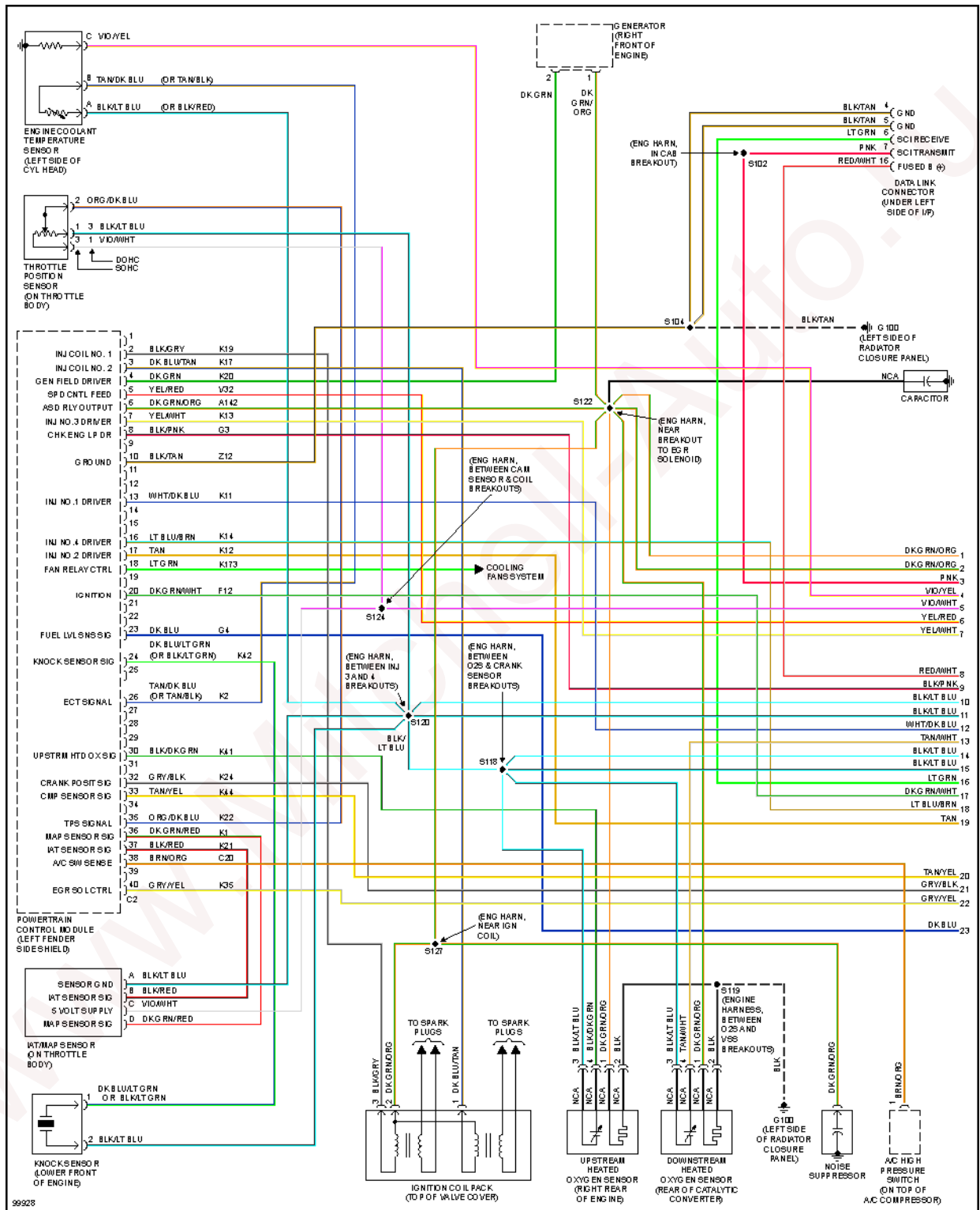


Fig. 8: 2.0L, Engine Performance Circuits (1 of 3)

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

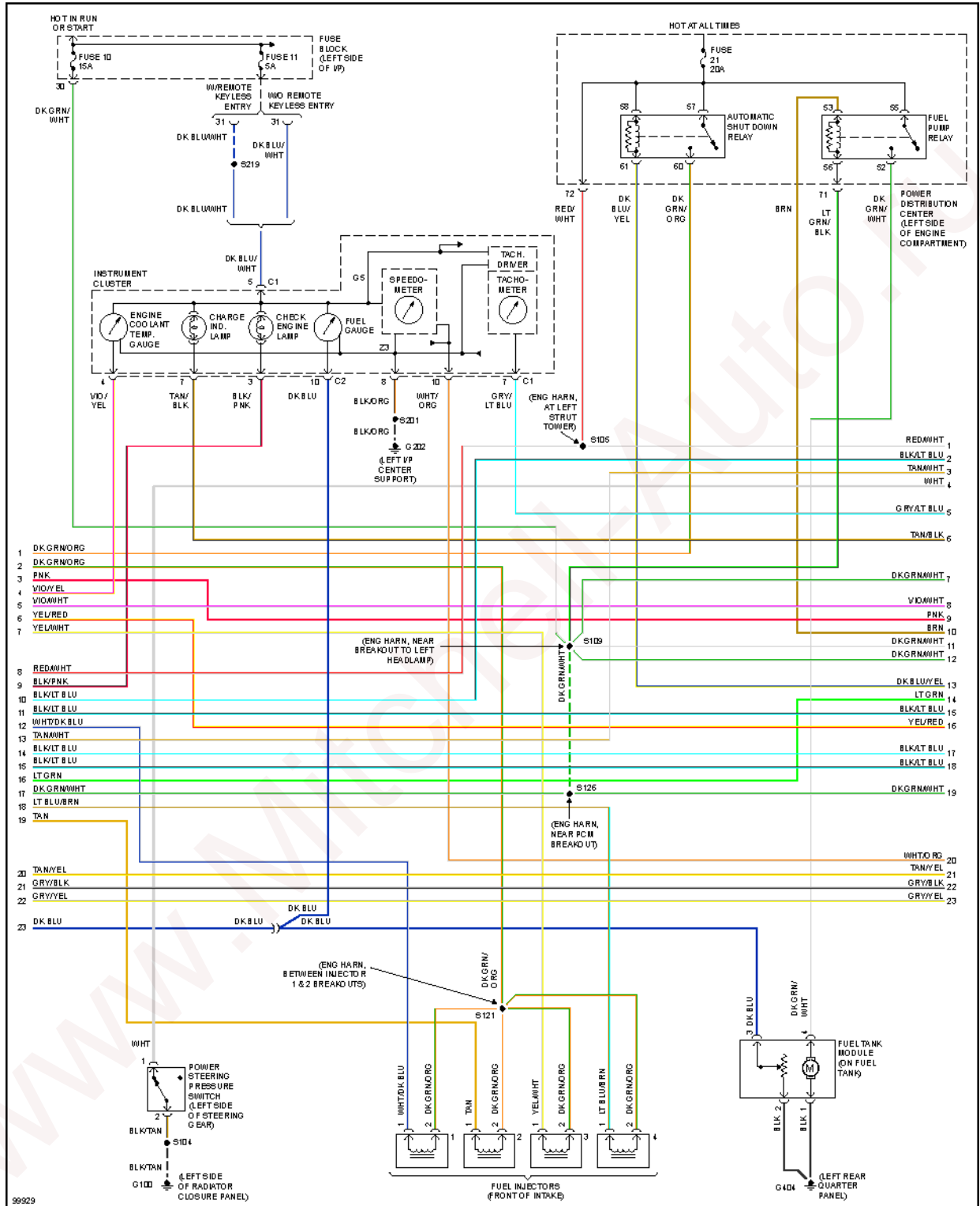


Fig. 9: 2.0L, Engine Performance Circuits (2 of 3)

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

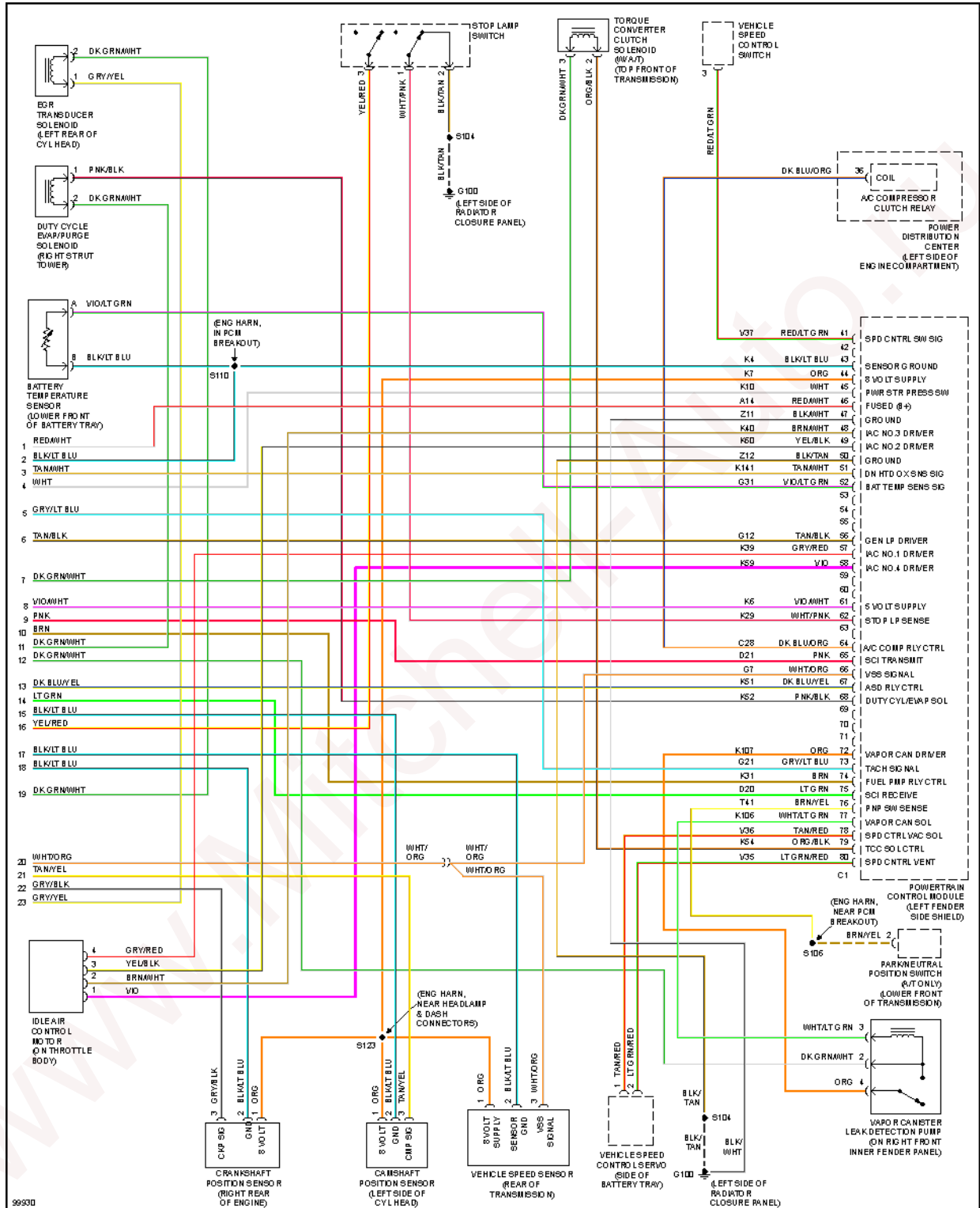


Fig. 10: 2.0L, Engine Performance Circuits (3 of 3)

EXTERIOR LIGHTS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

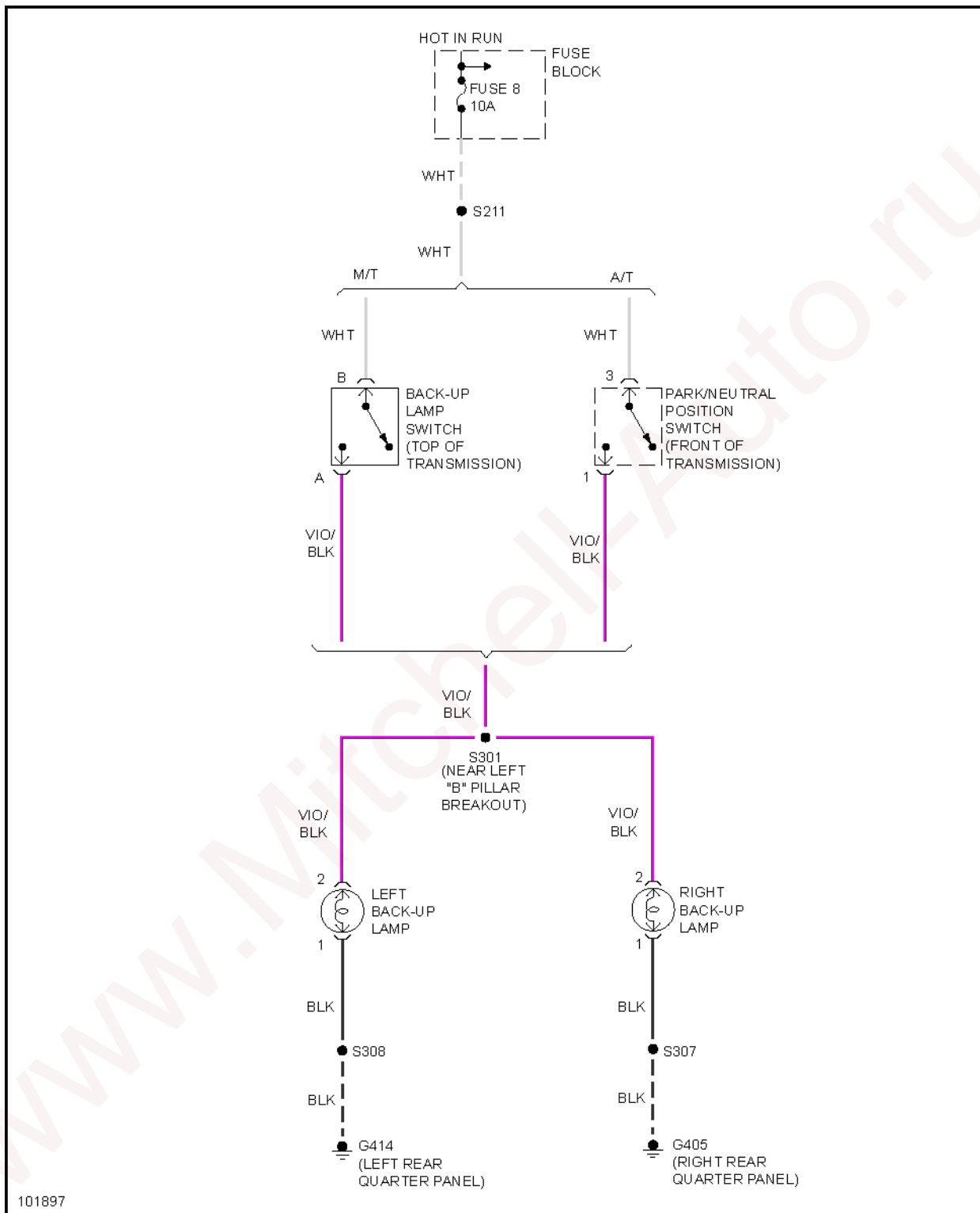


Fig. 11: Back-up Lamps Circuit

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

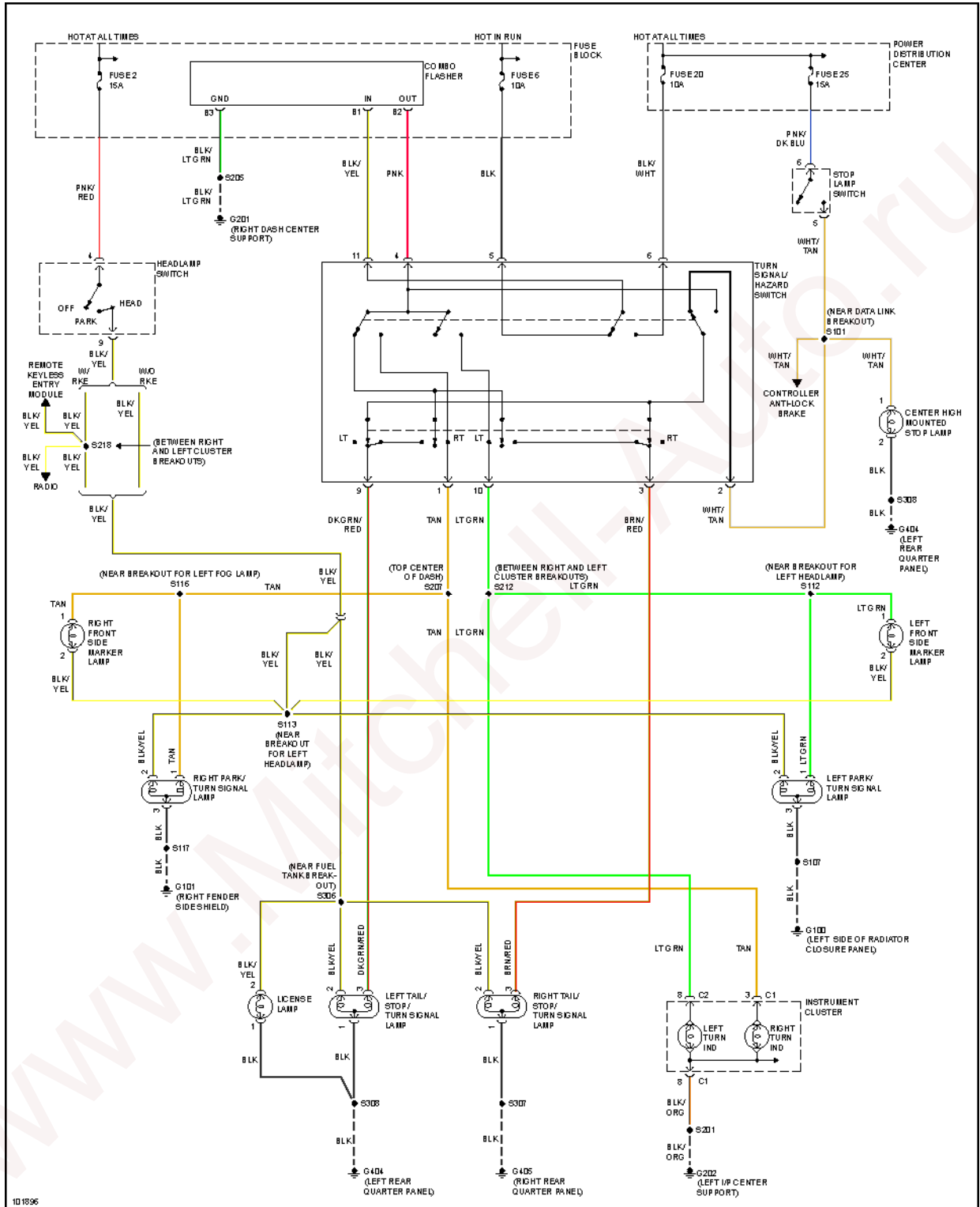


Fig. 12: Exterior Lamps Circuit

GROUND DISTRIBUTION

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

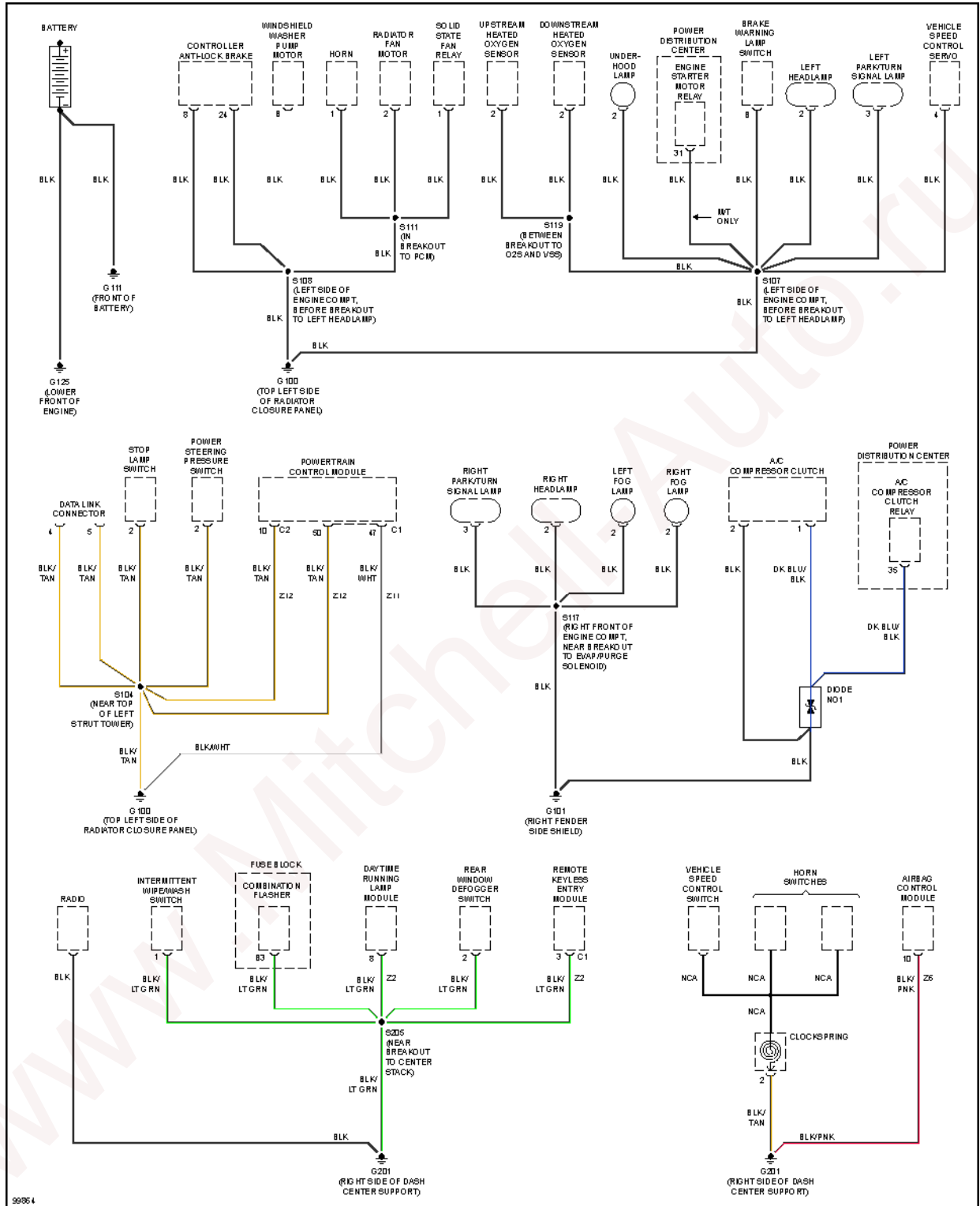


Fig. 13: Ground Distribution Circuit (1 of 2)

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

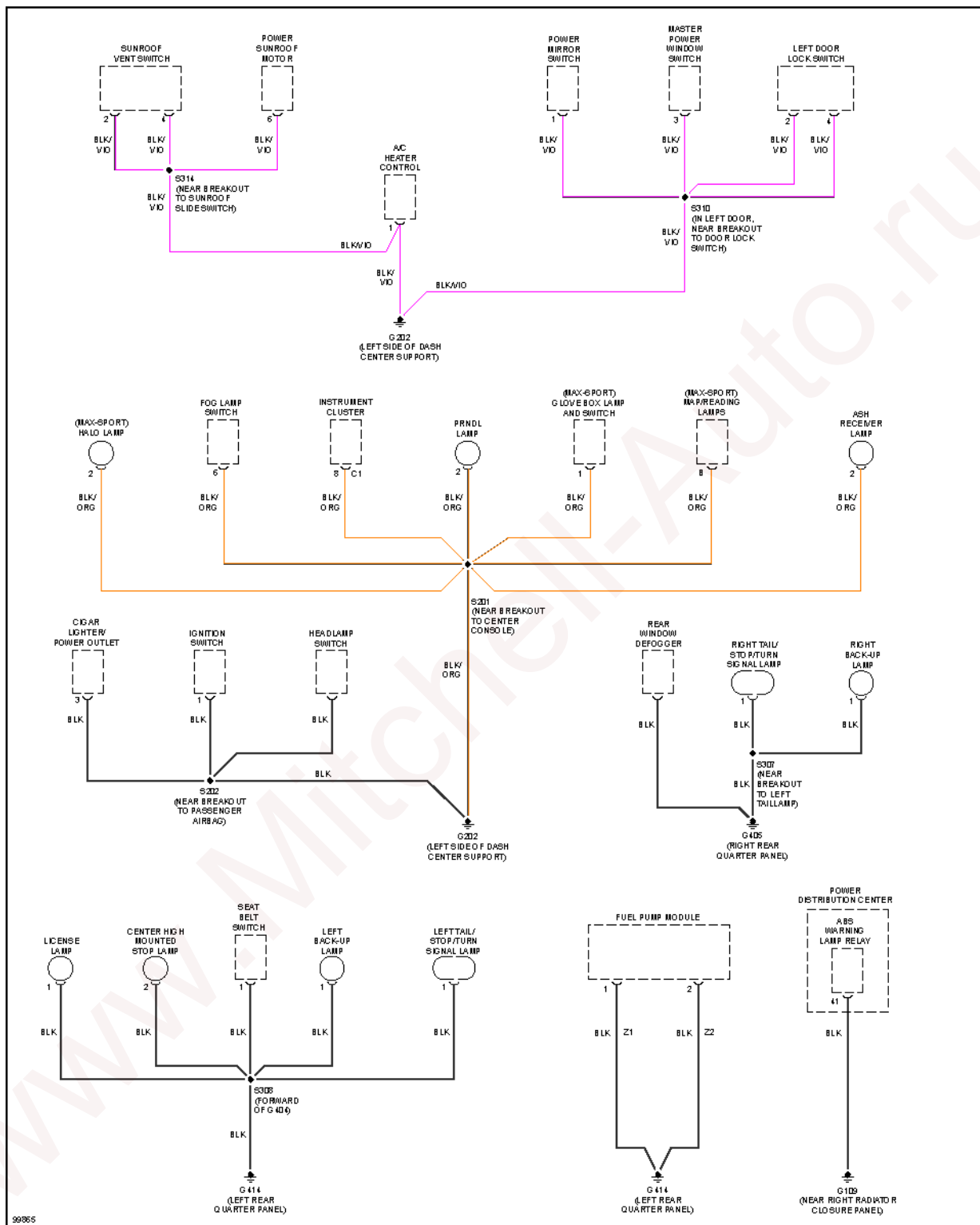


Fig. 14: Ground Distribution Circuit (2 of 2)

HEADLIGHTS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

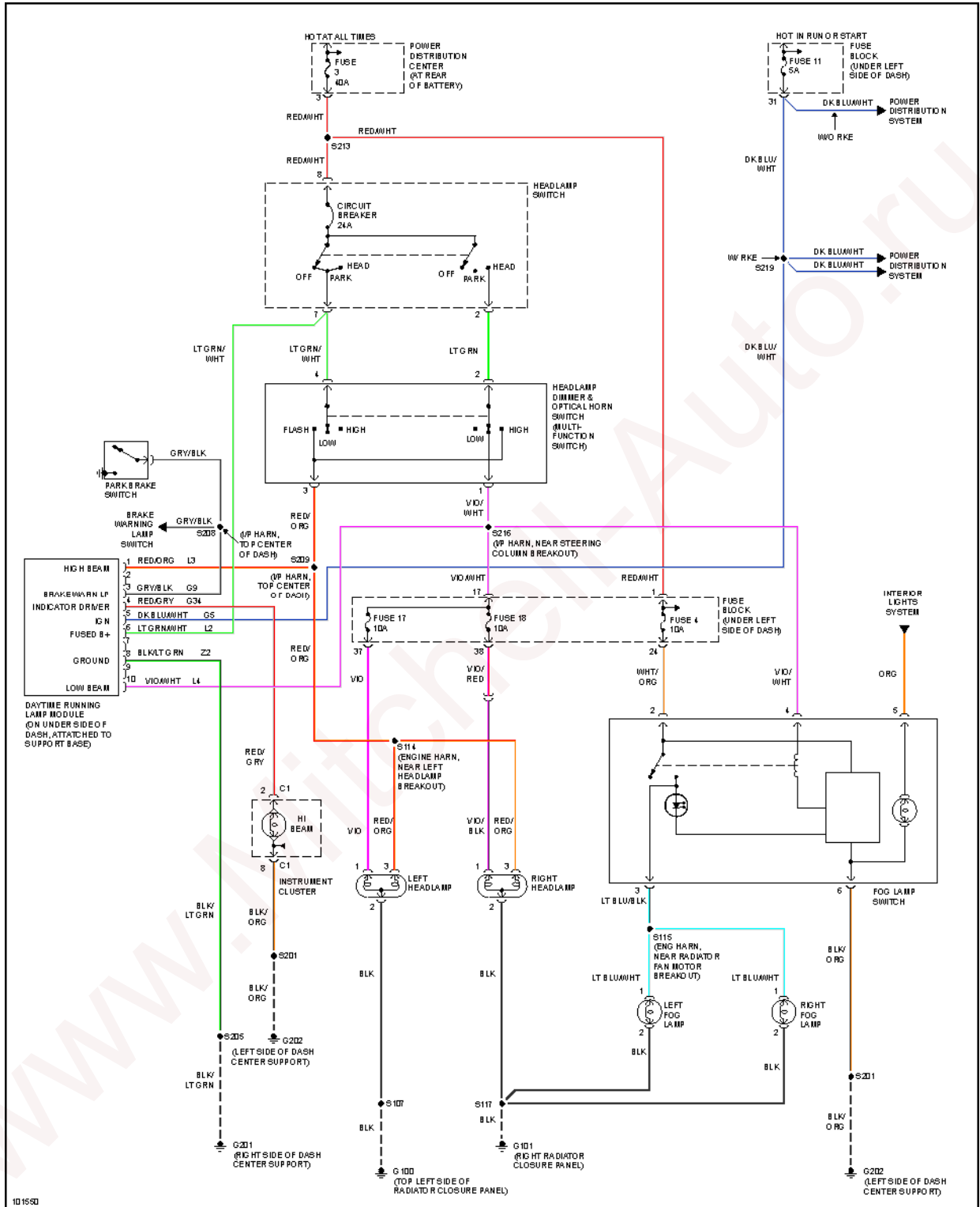


Fig. 15: Headlamps/Fog Lamps Circuit, W/ DRL

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

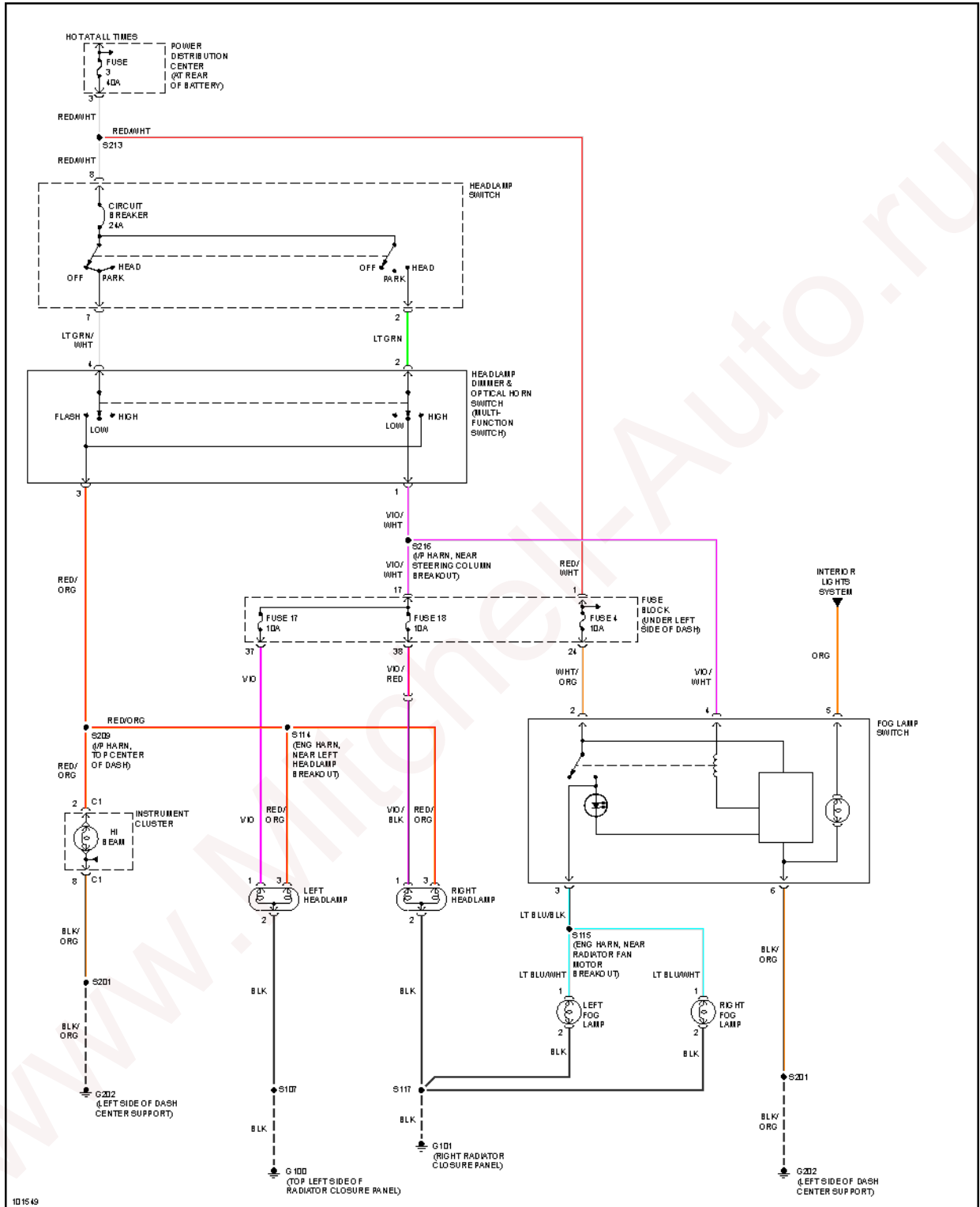


Fig. 16: Headlamps/Fog Lamps Circuit, W/O DRL

HORN

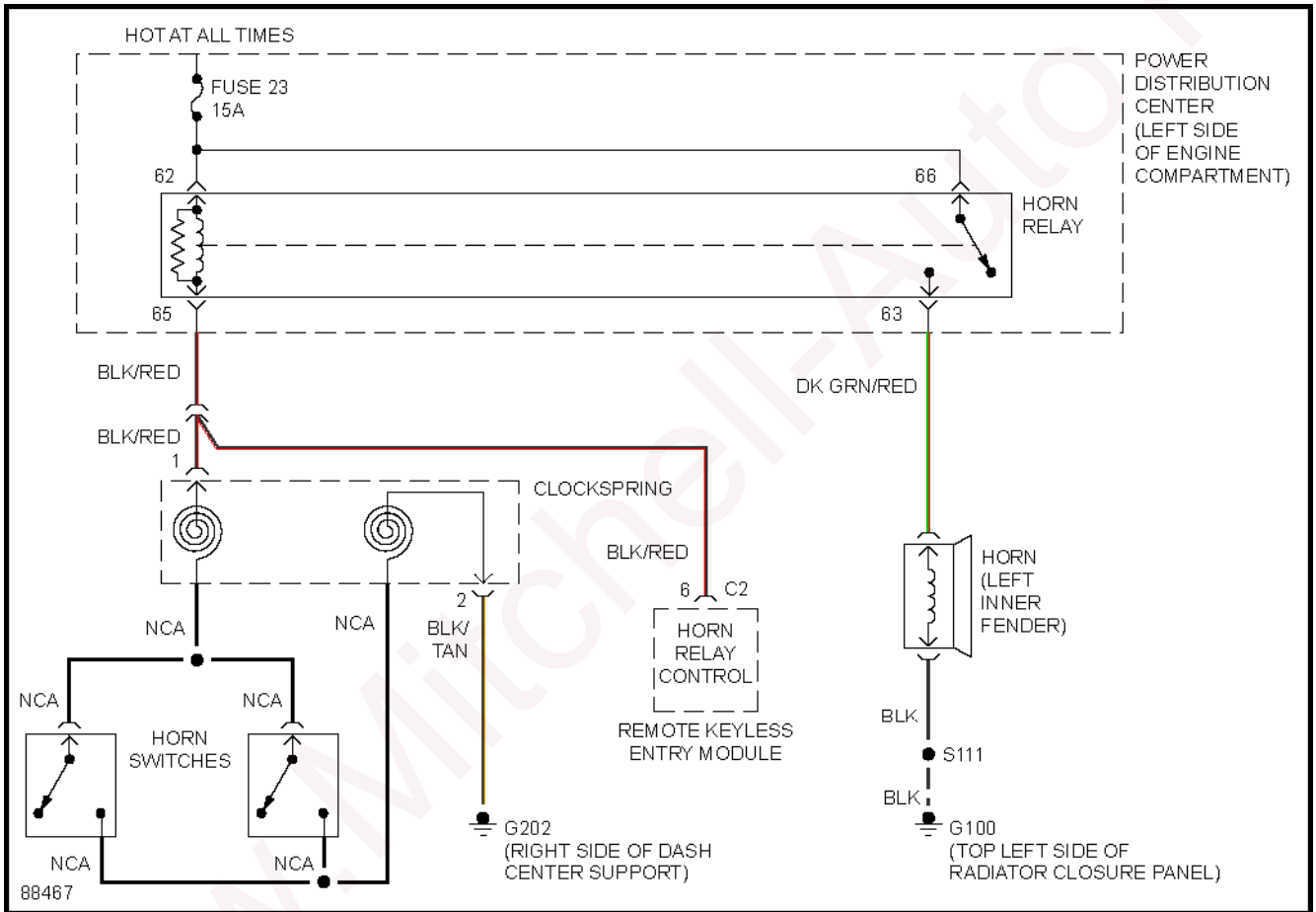


Fig. 17: Horn Circuit

INSTRUMENT CLUSTER

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

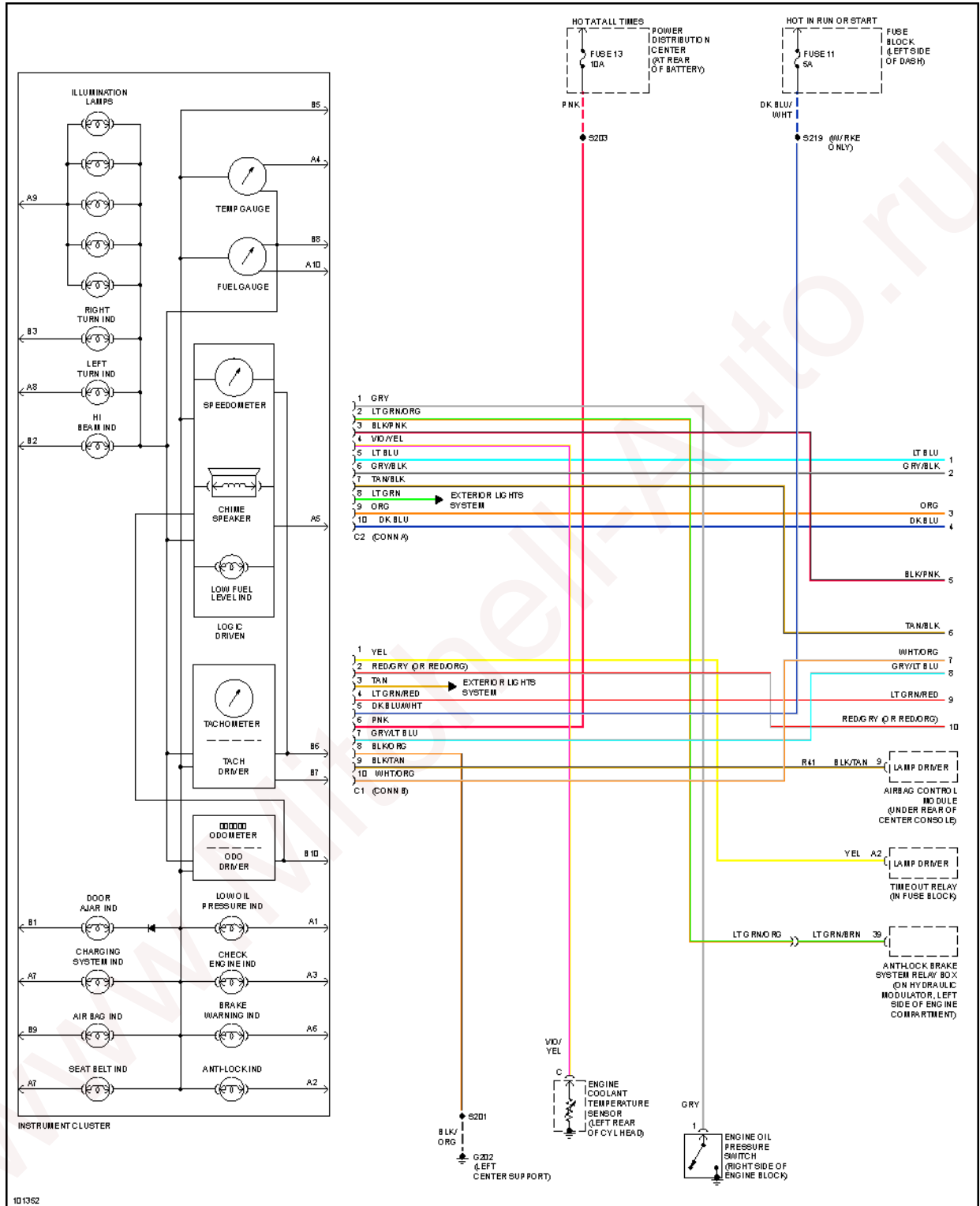


Fig. 18: Instrument Cluster Circuit (1 of 2)

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

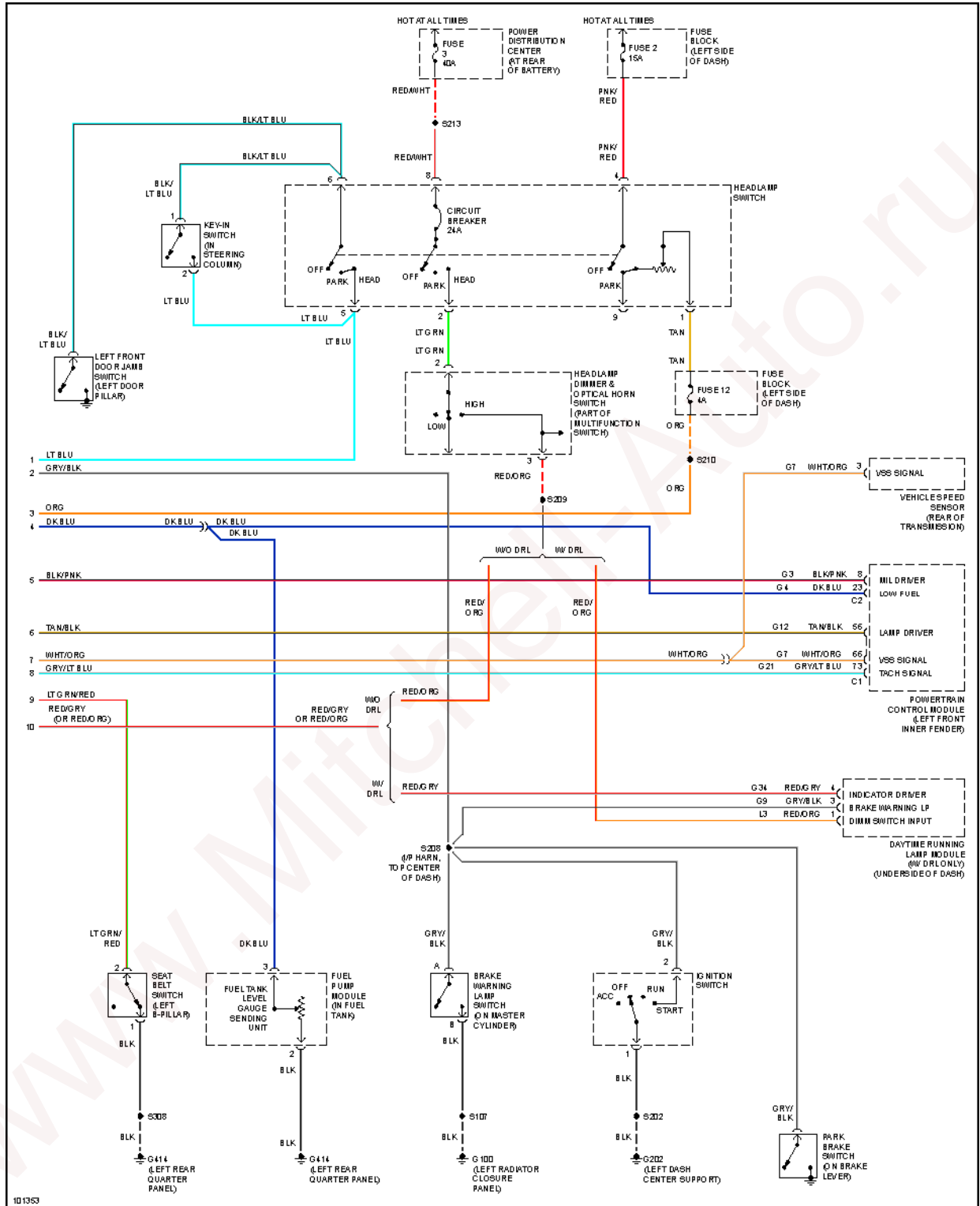


Fig. 19: Instrument Cluster Circuit (2 of 2)

INTERIOR LIGHTS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

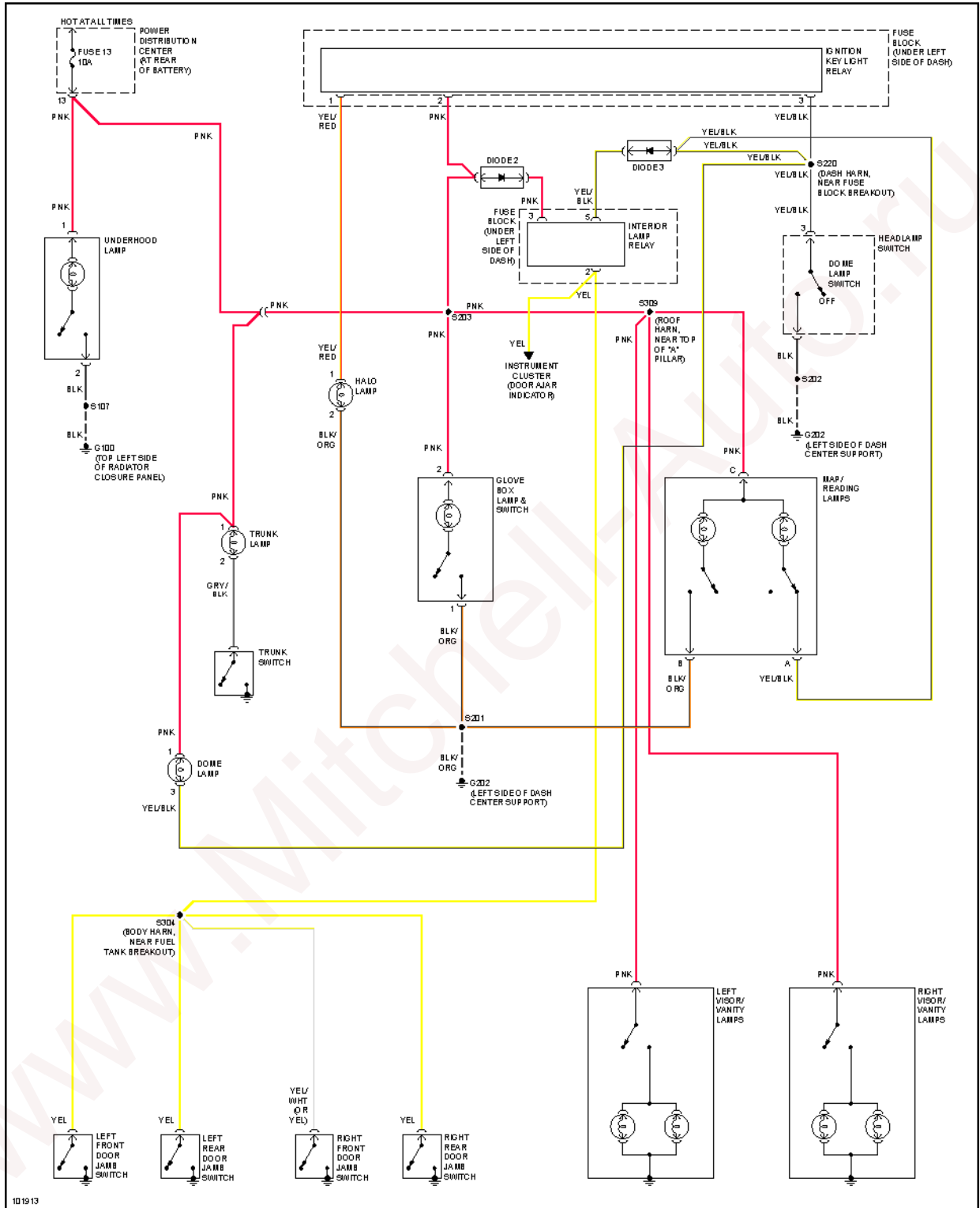


Fig. 20: Courtesy Lamp Circuit

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

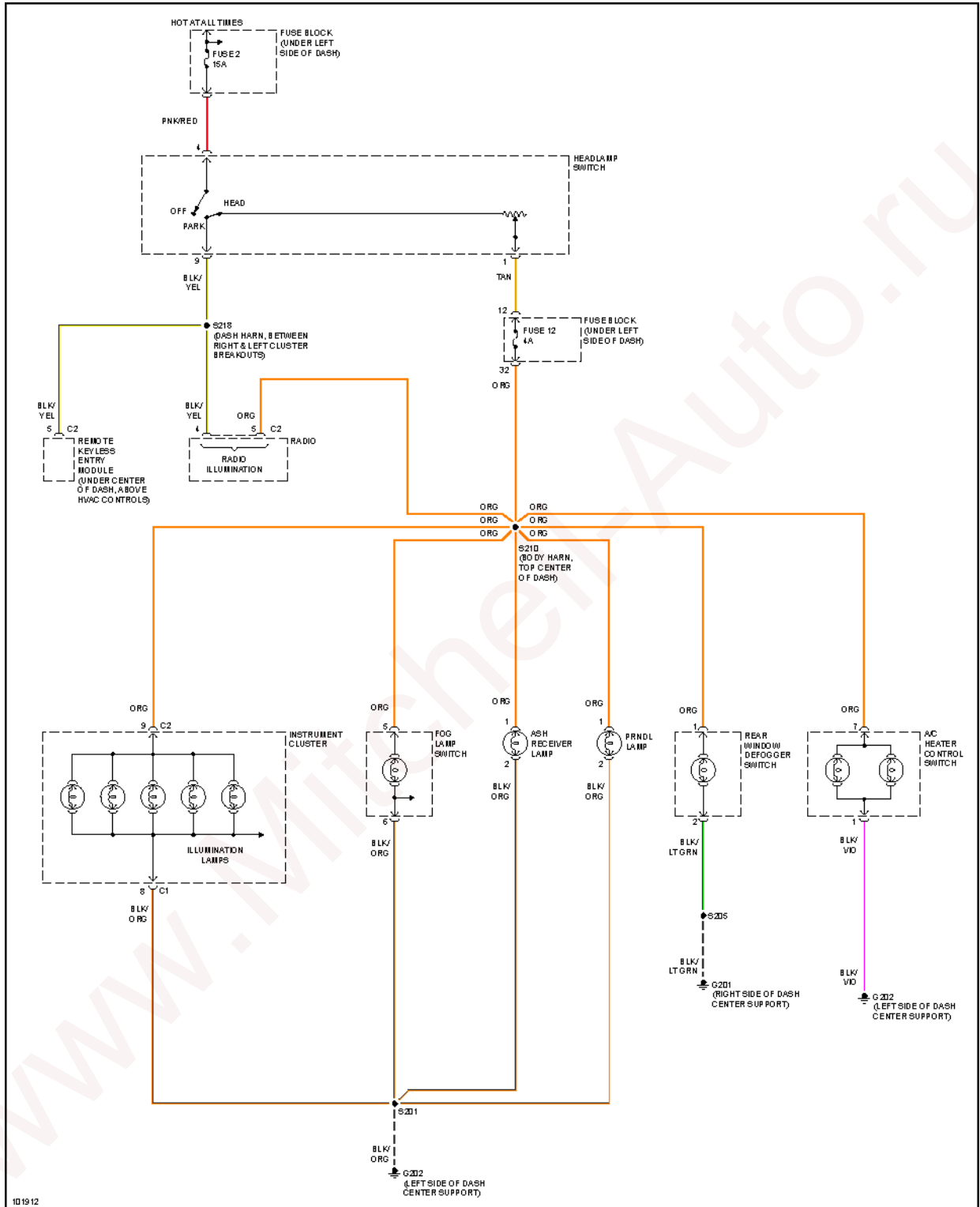


Fig. 21: Instrument Illumination Circuit

POWER DISTRIBUTION

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

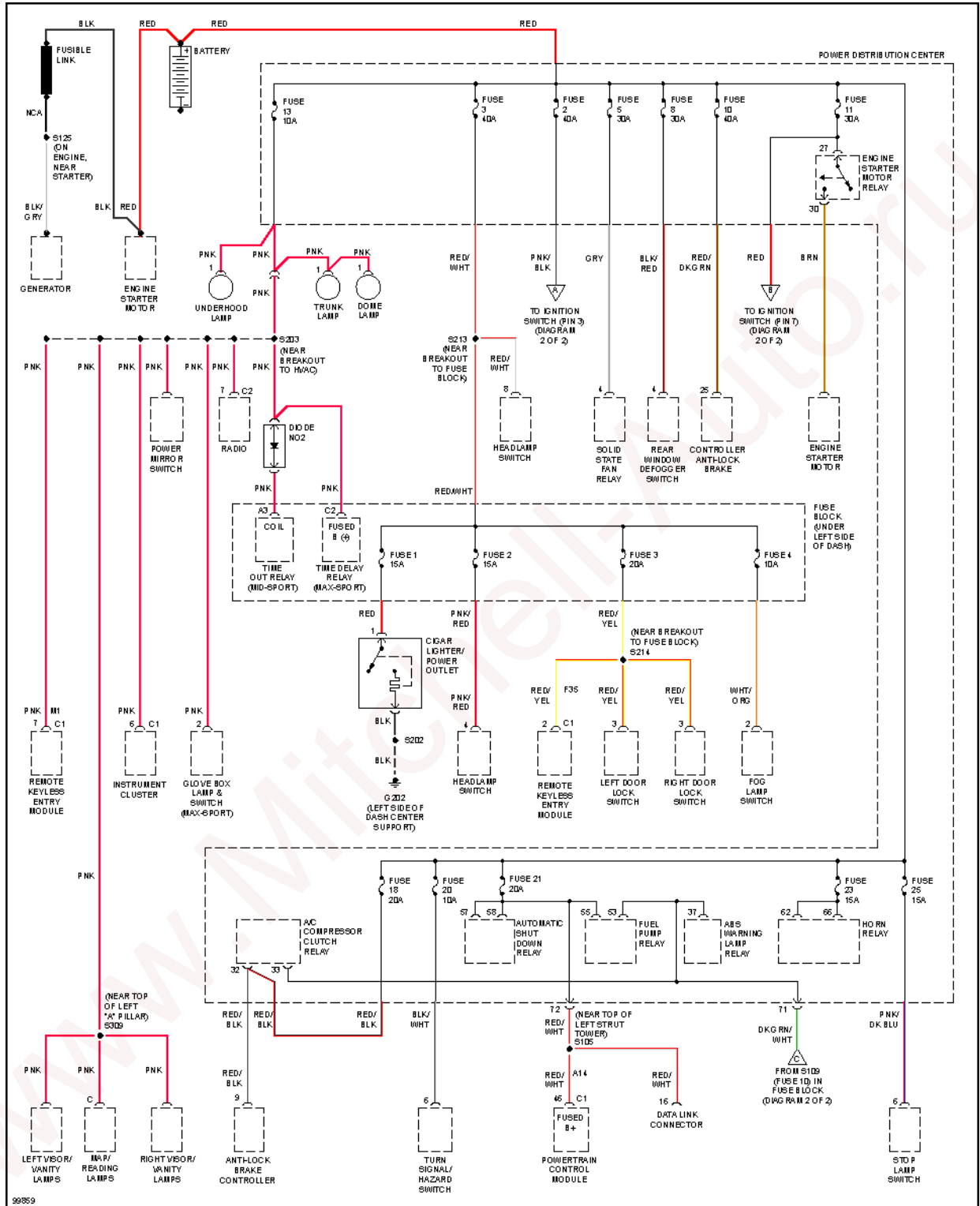


Fig. 22: Power Distribution Circuit (1 of 2)

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

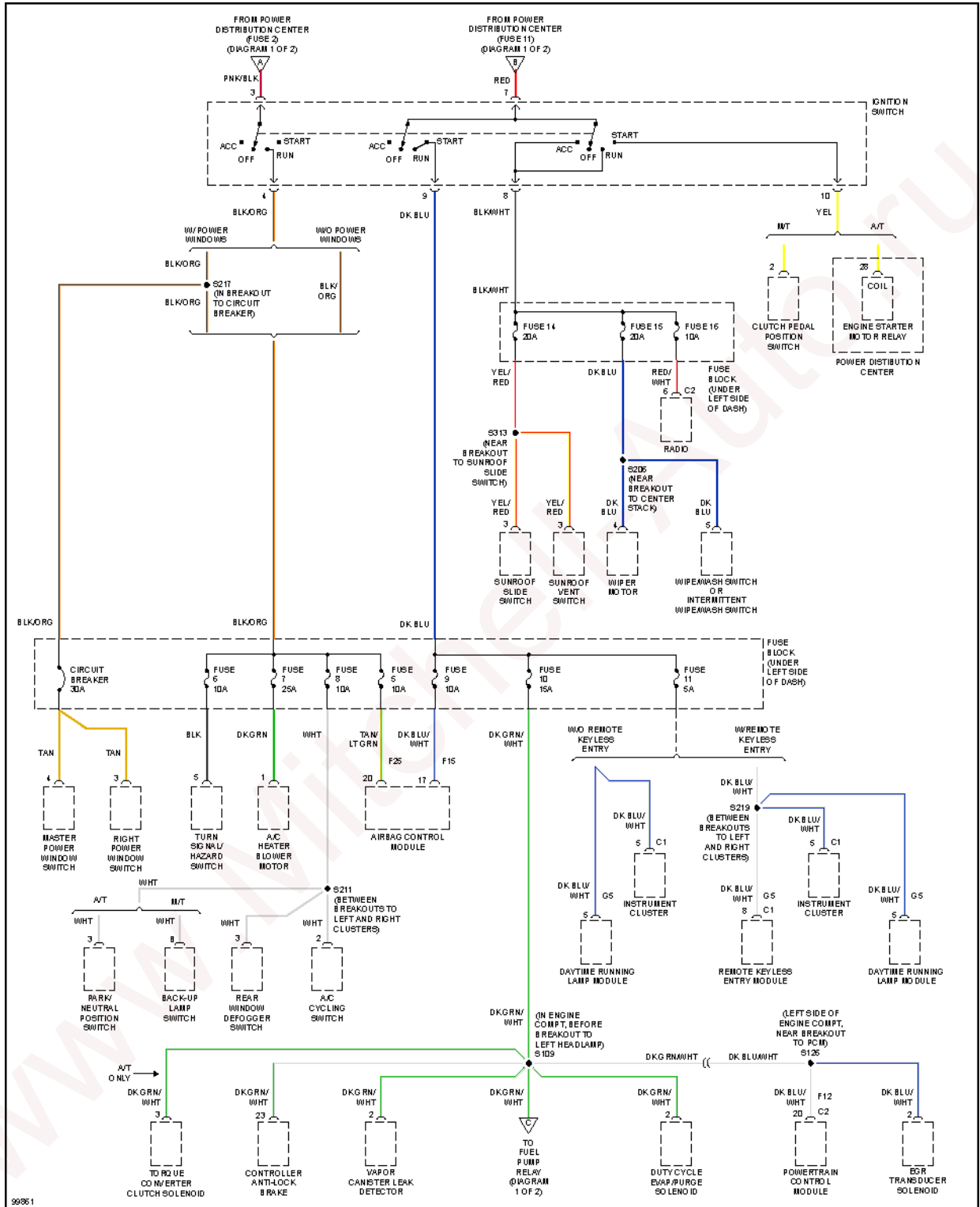


Fig. 23: Power Distribution Circuit (2 of 2)

POWER DOOR LOCKS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

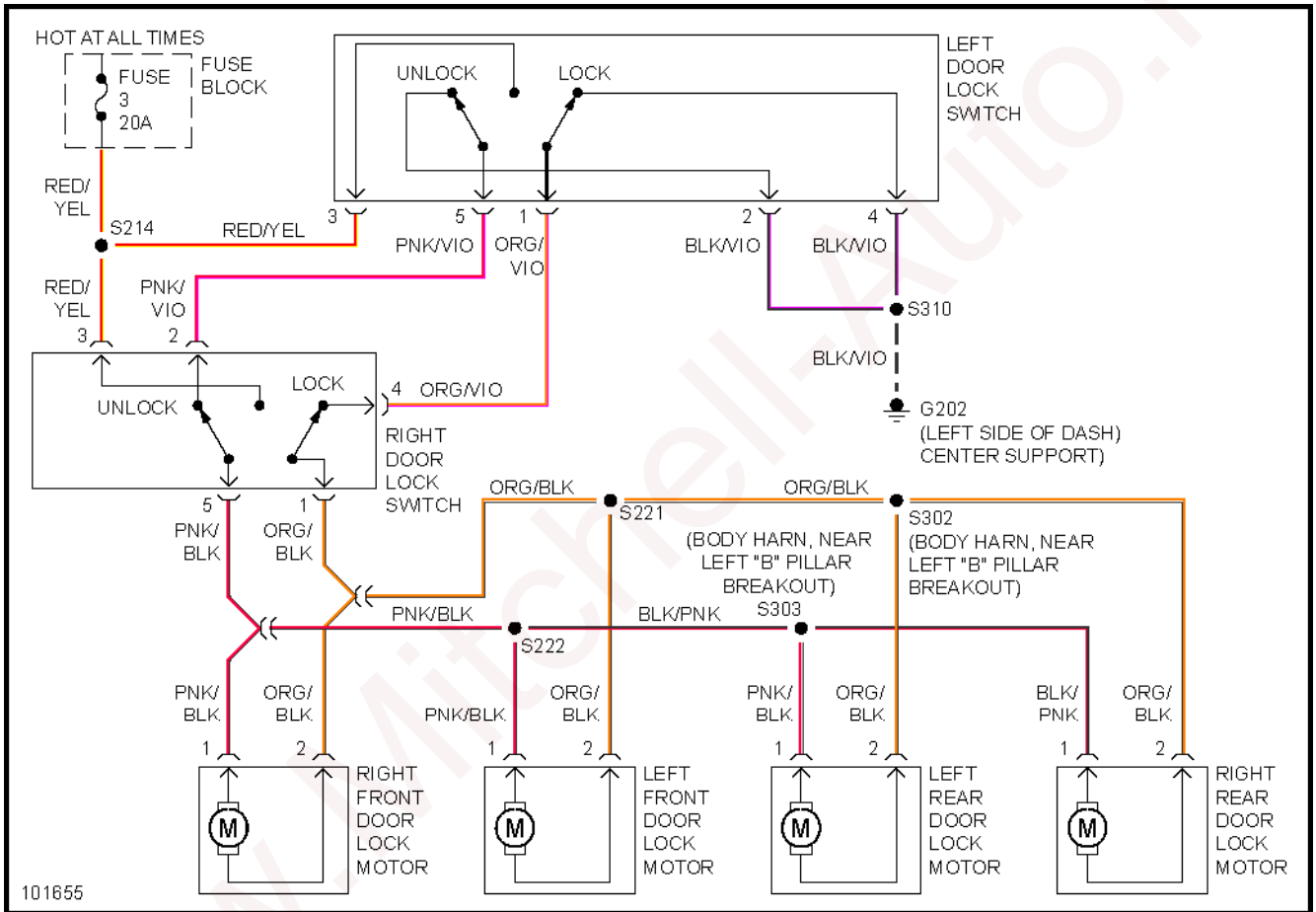


Fig. 24: Door Lock Circuit

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

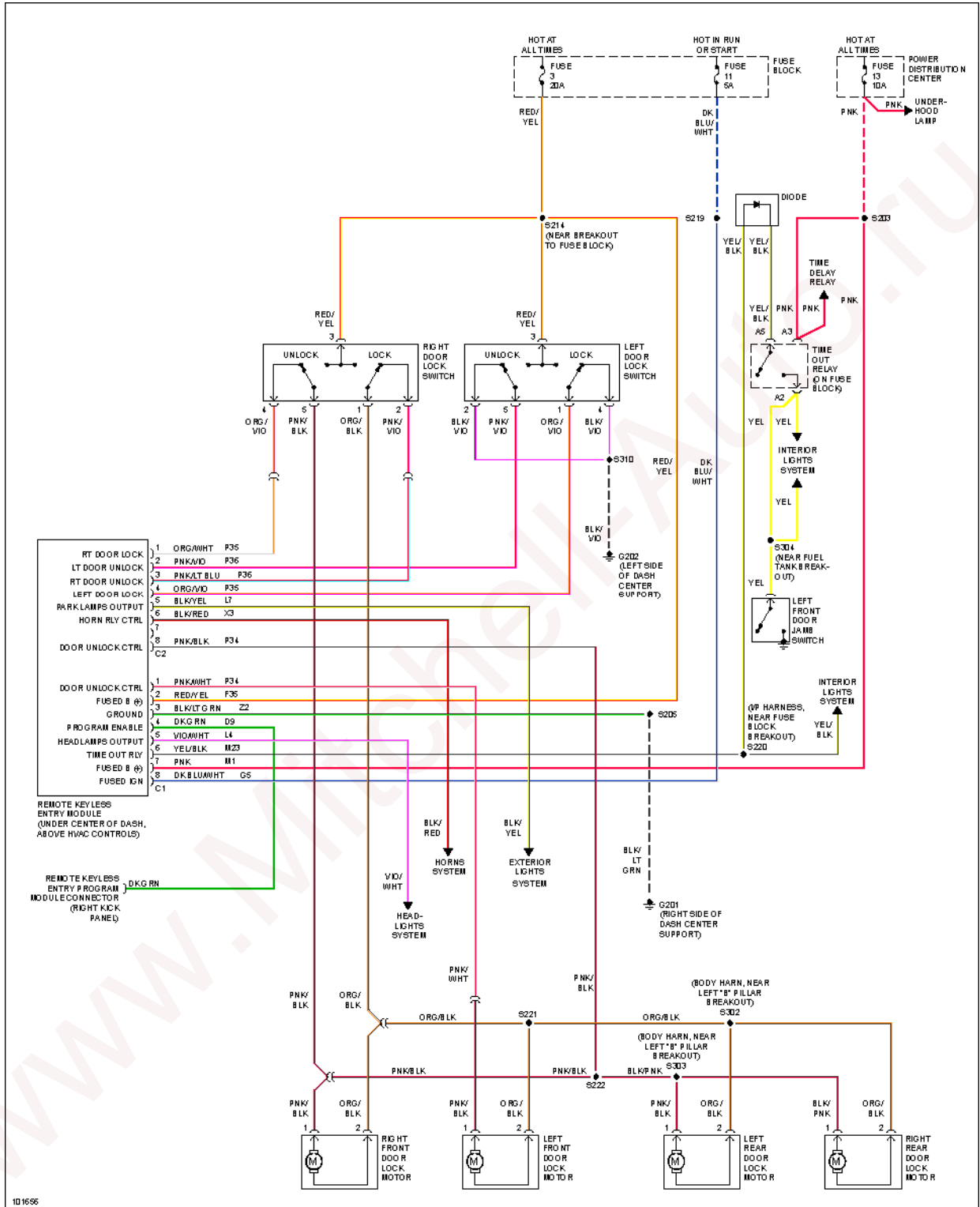


Fig. 25: Keyless Entry Circuit

POWER MIRRORS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

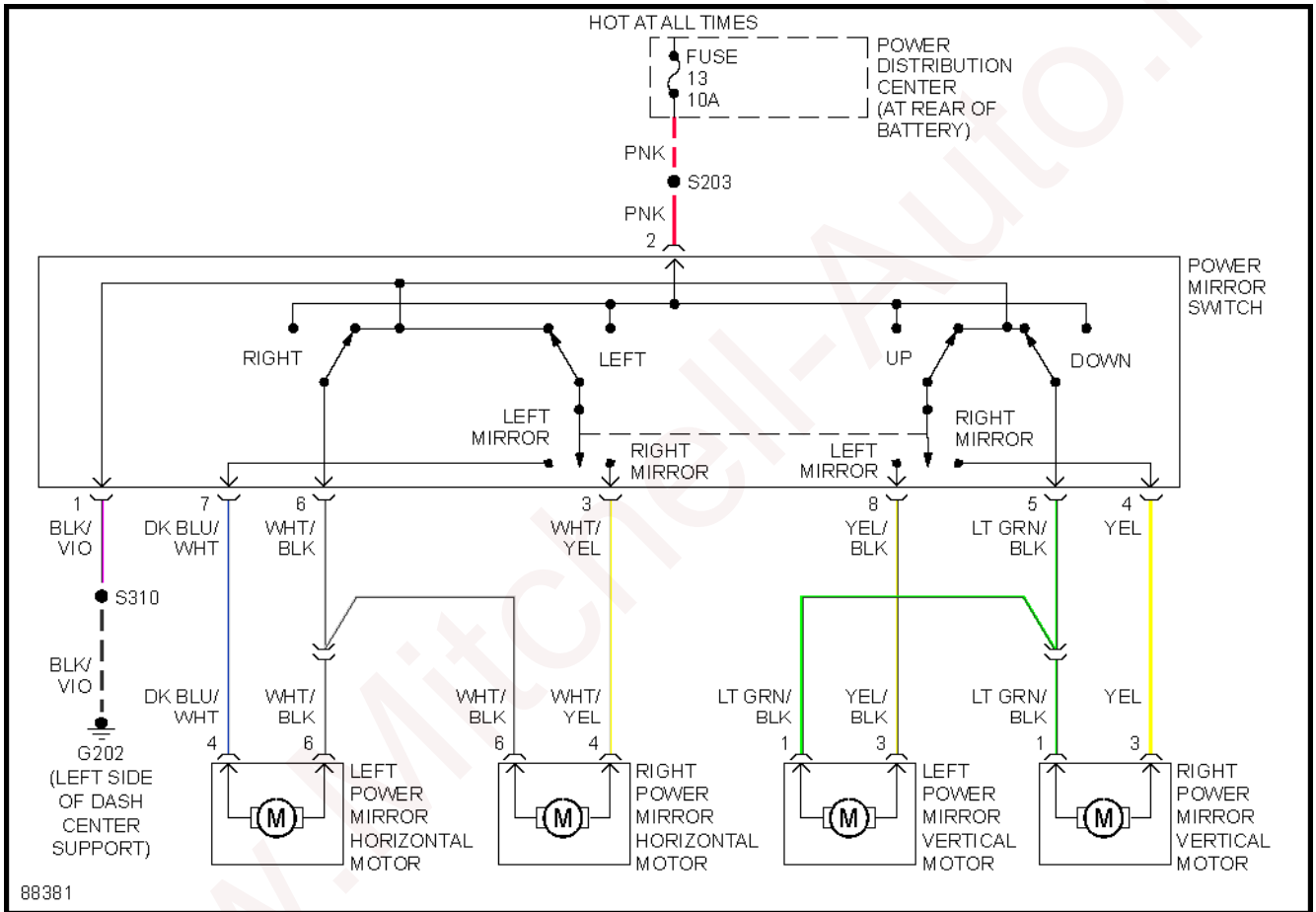


Fig. 26: Power Mirror Circuit

POWER TOP/SUNROOF

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

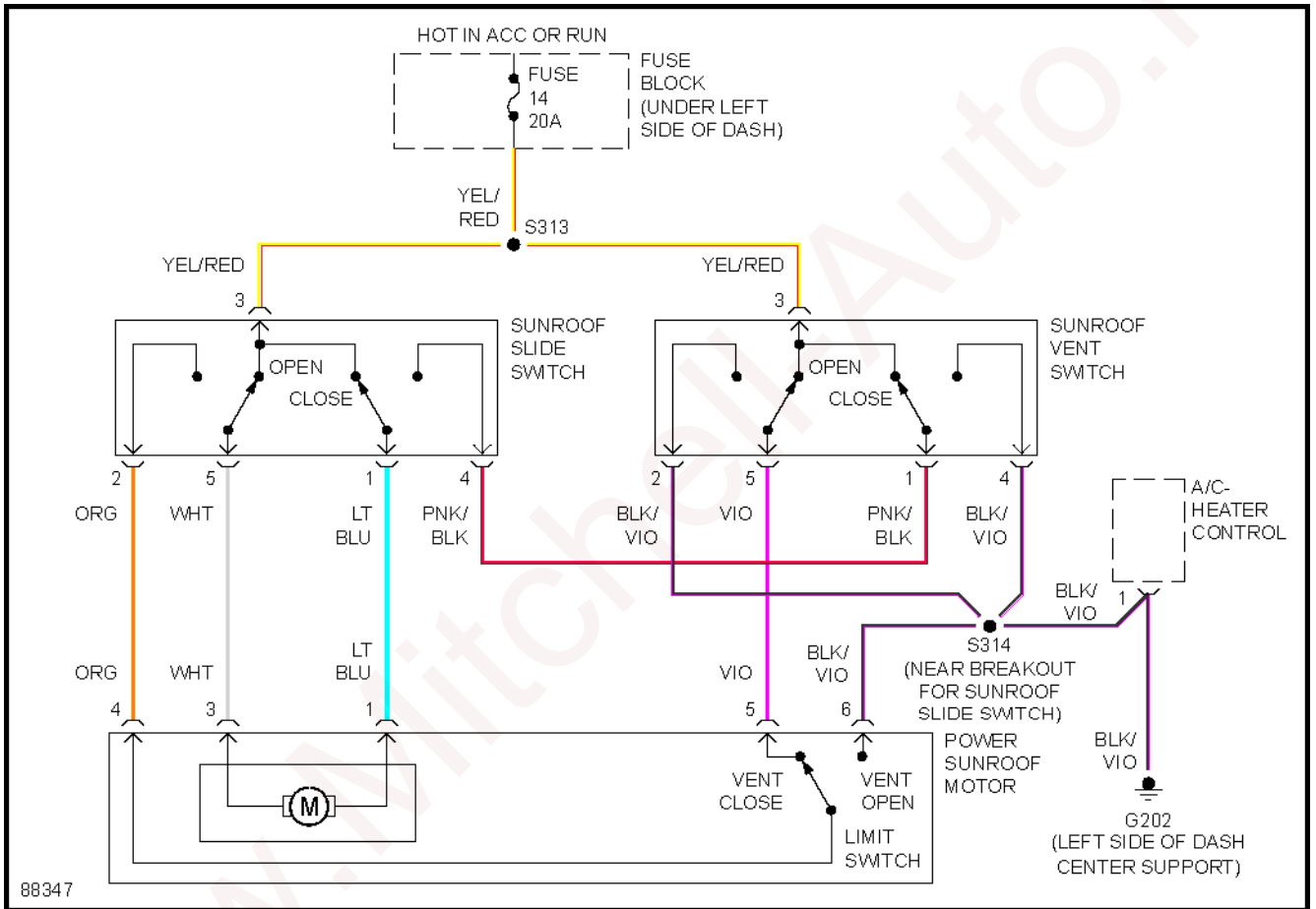


Fig. 27: Power Top/Sunroof Circuits

POWER WINDOWS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

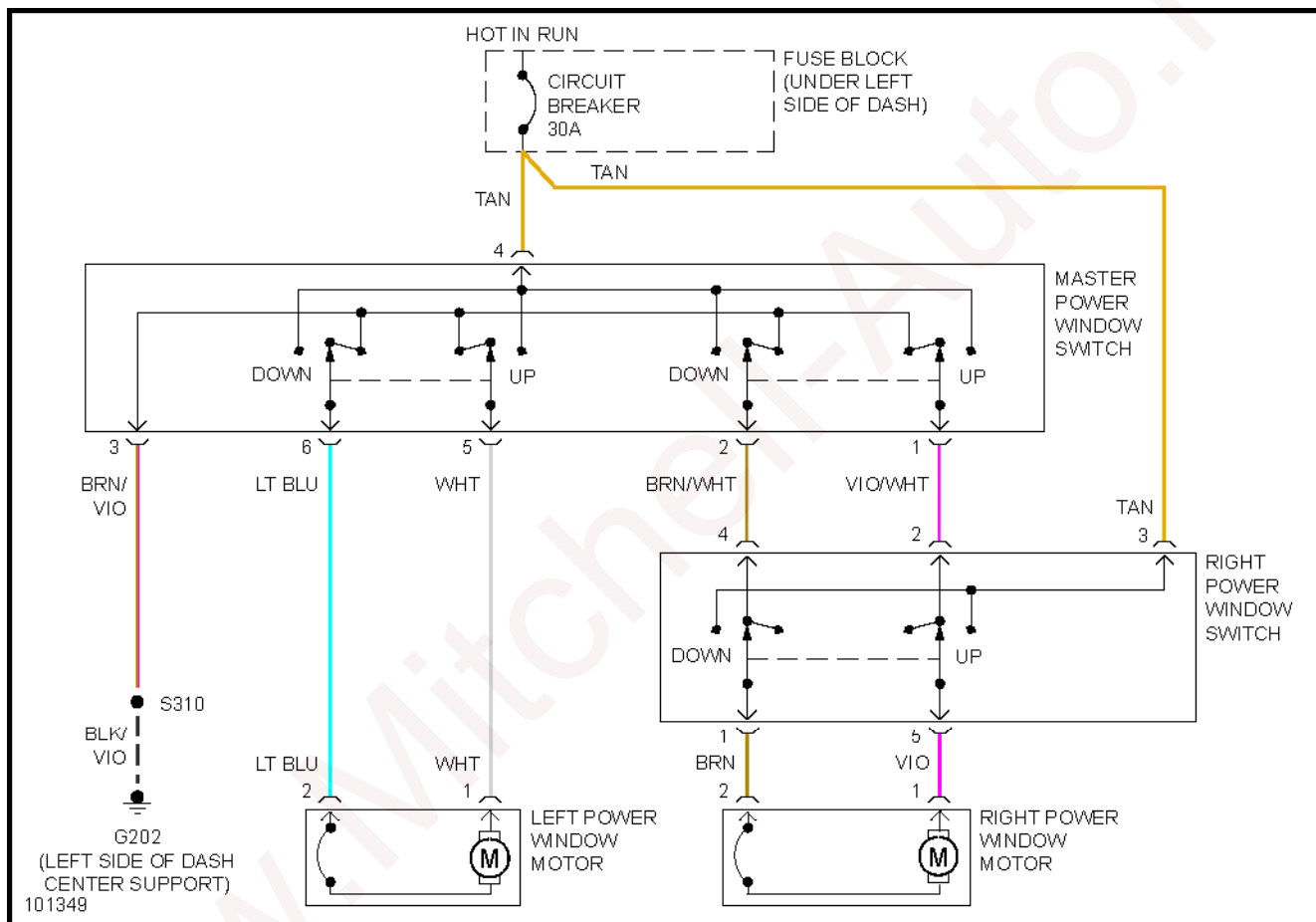


Fig. 28: Power Window Circuit

RADIO

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

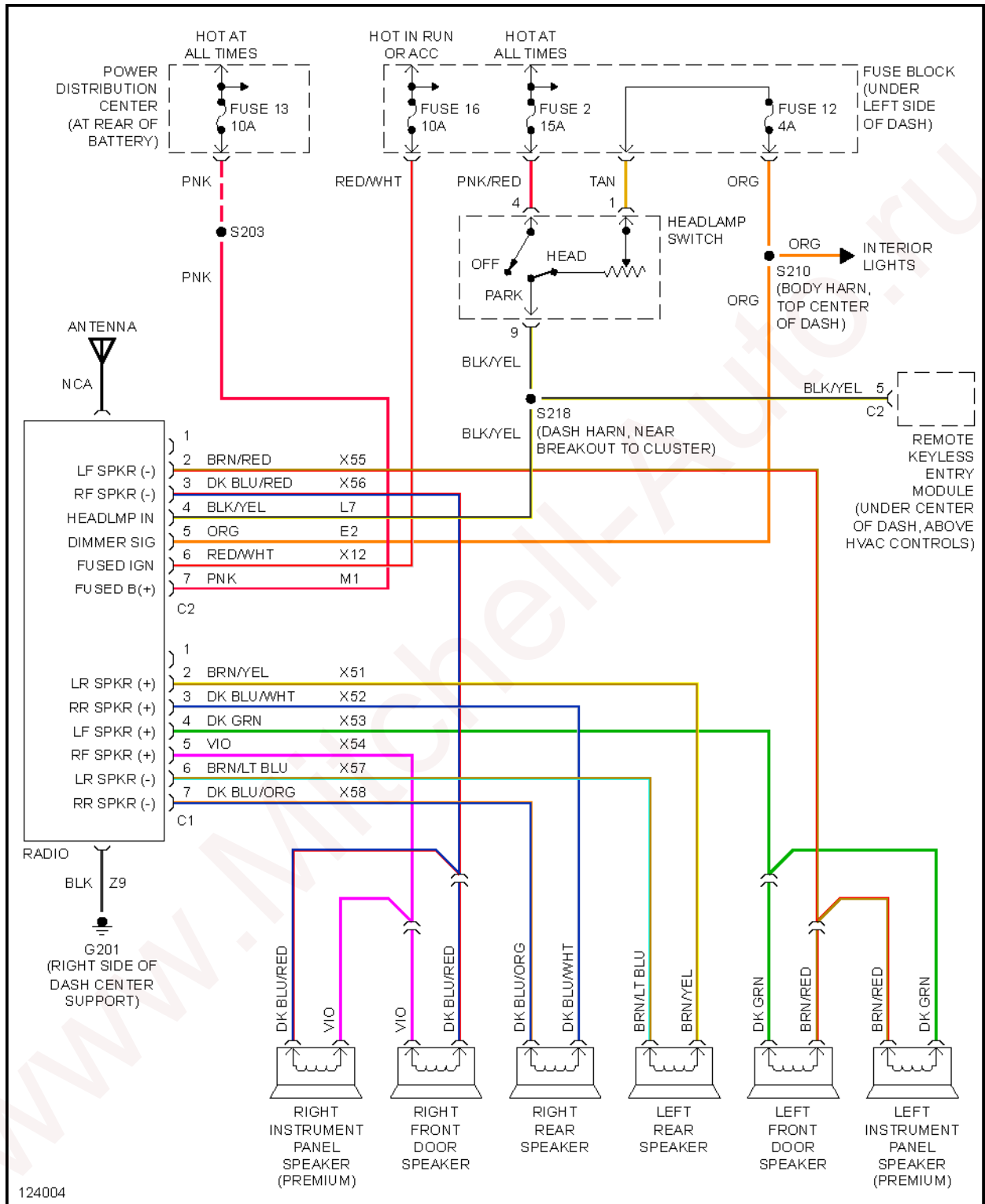


Fig. 29: Radio Circuits

STARTING/CHARGING

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

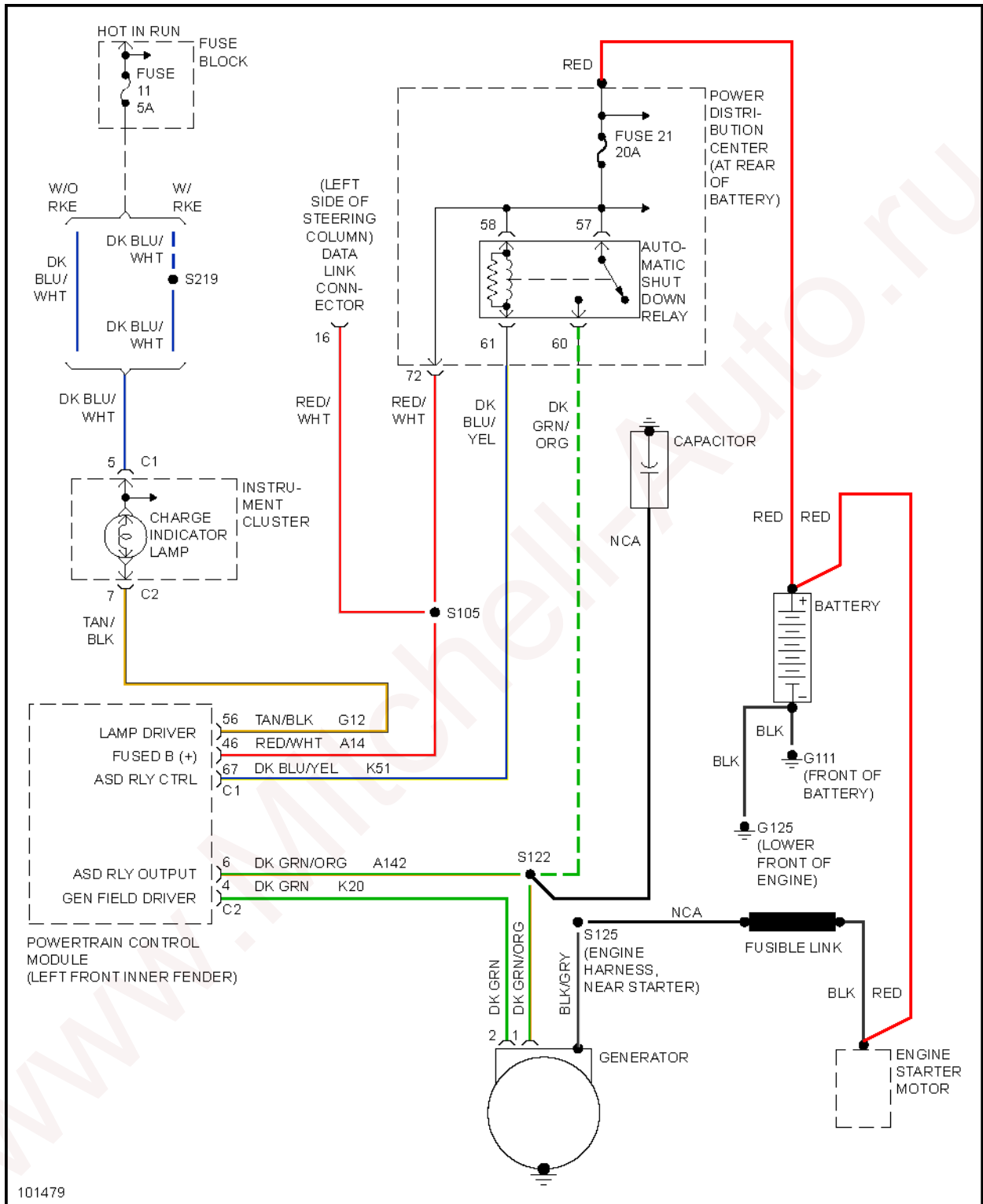


Fig. 30: Charging Circuit

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

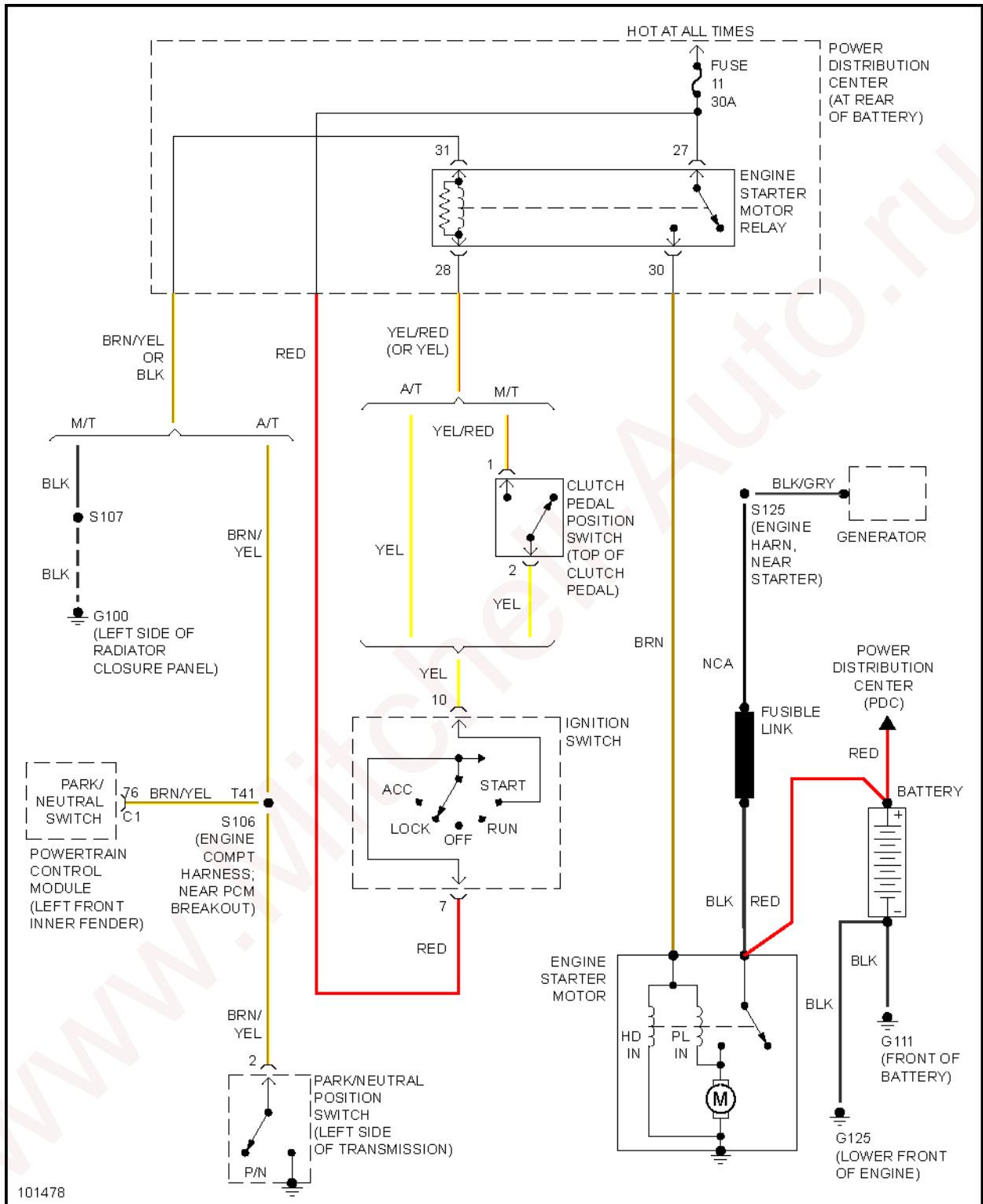


Fig. 31: Starting Circuit

SUPPLEMENTAL RESTRAINTS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

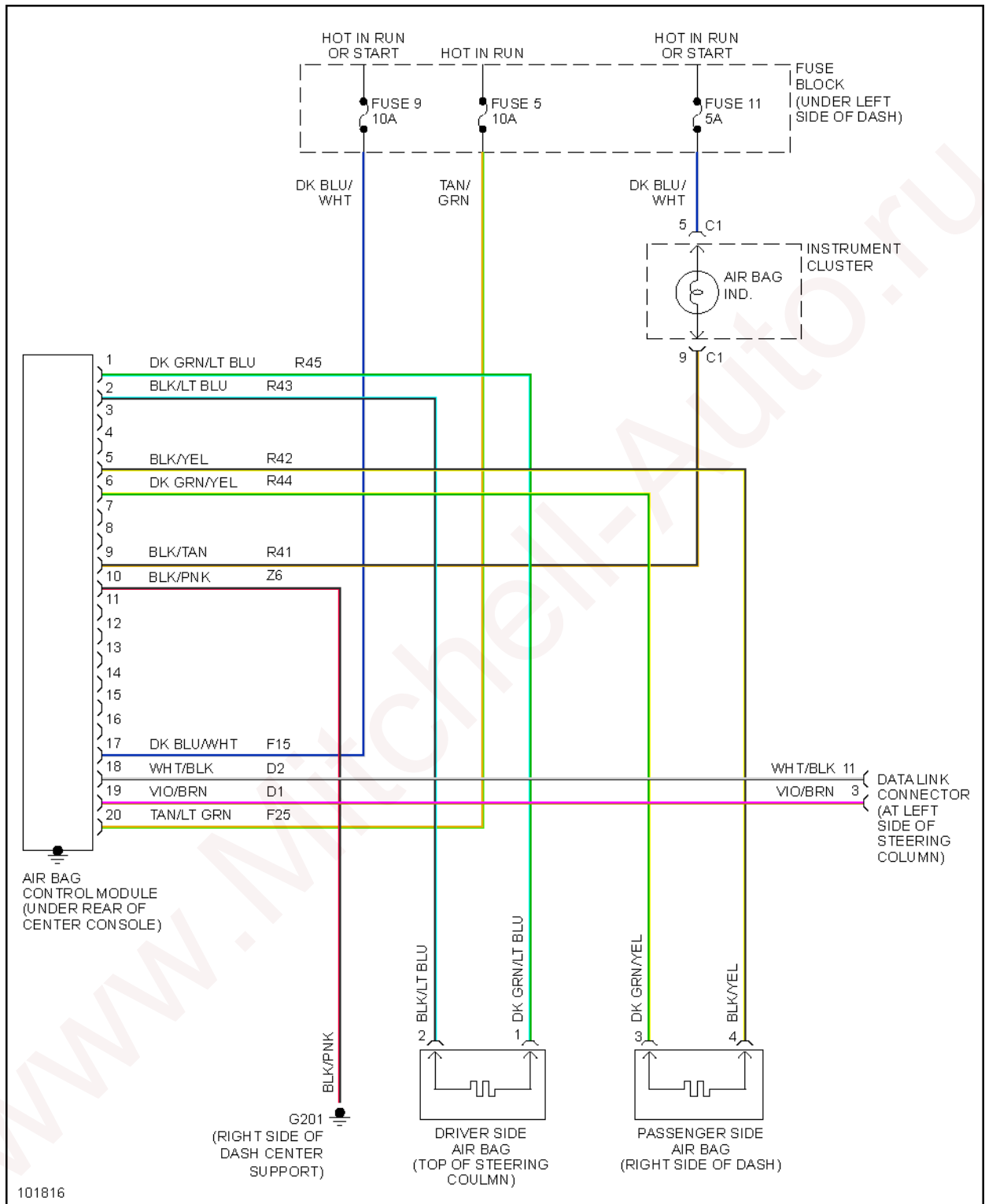


Fig. 32: Supplemental Restraint Circuit

TRANSMISSION

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

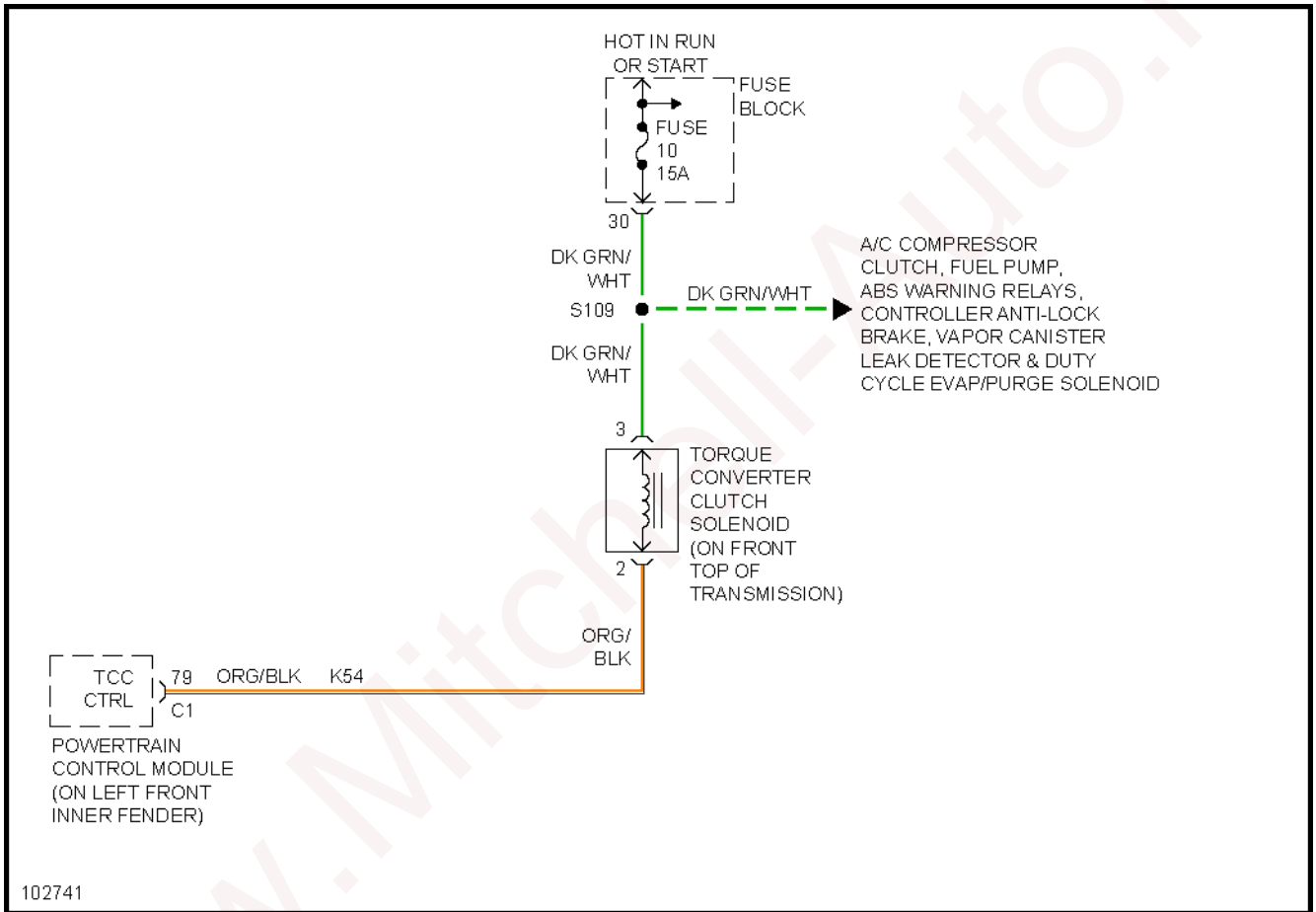


Fig. 33: Transmission Circuit

WARNING SYSTEMS

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

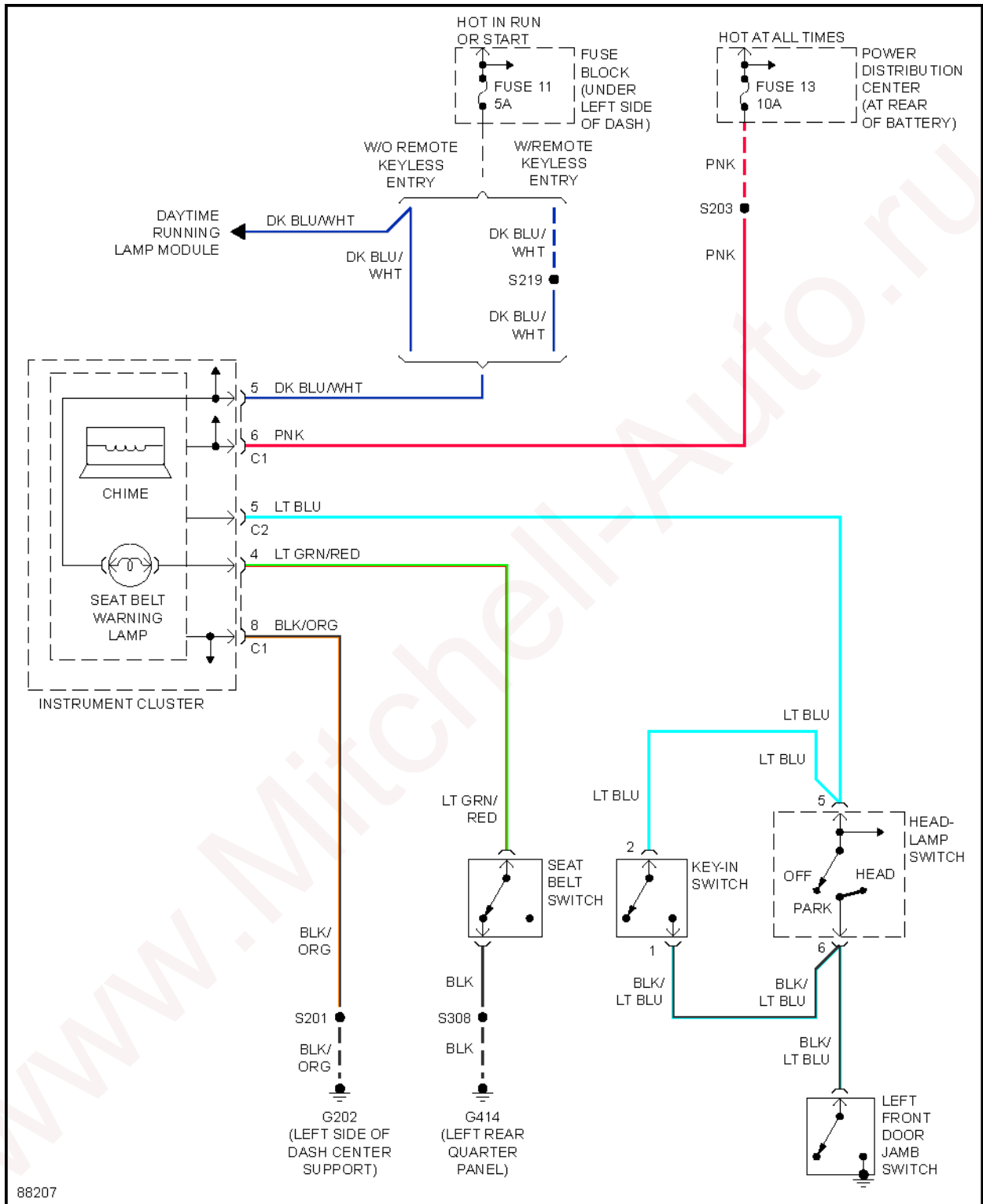


Fig. 34: Warning System Circuits

WIPER/WASHER

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

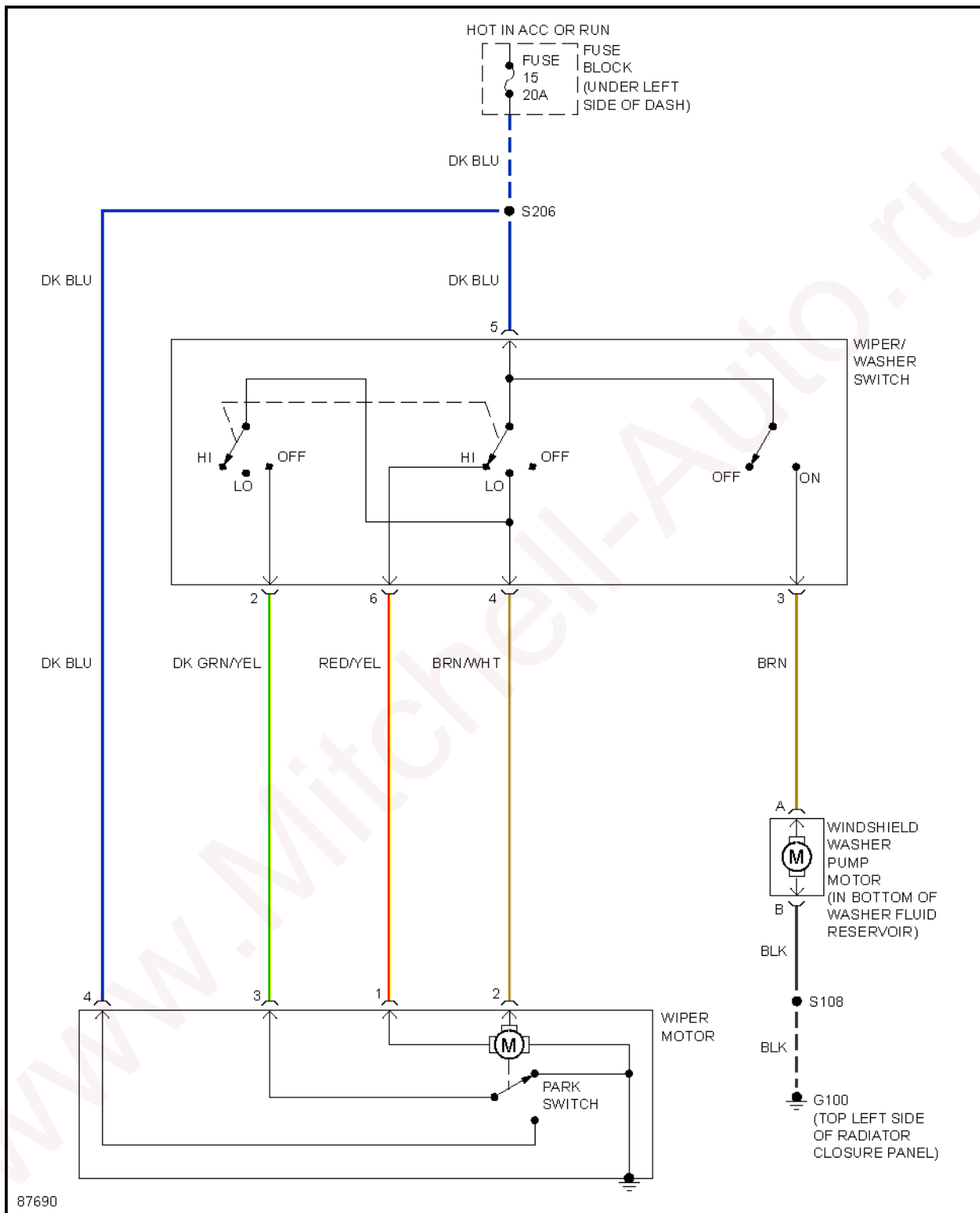


Fig. 35: 2-Speed Wiper/Washer Circuit

1998 Dodge Neon Sport

1998 System Wiring Diagrams Dodge - Neon

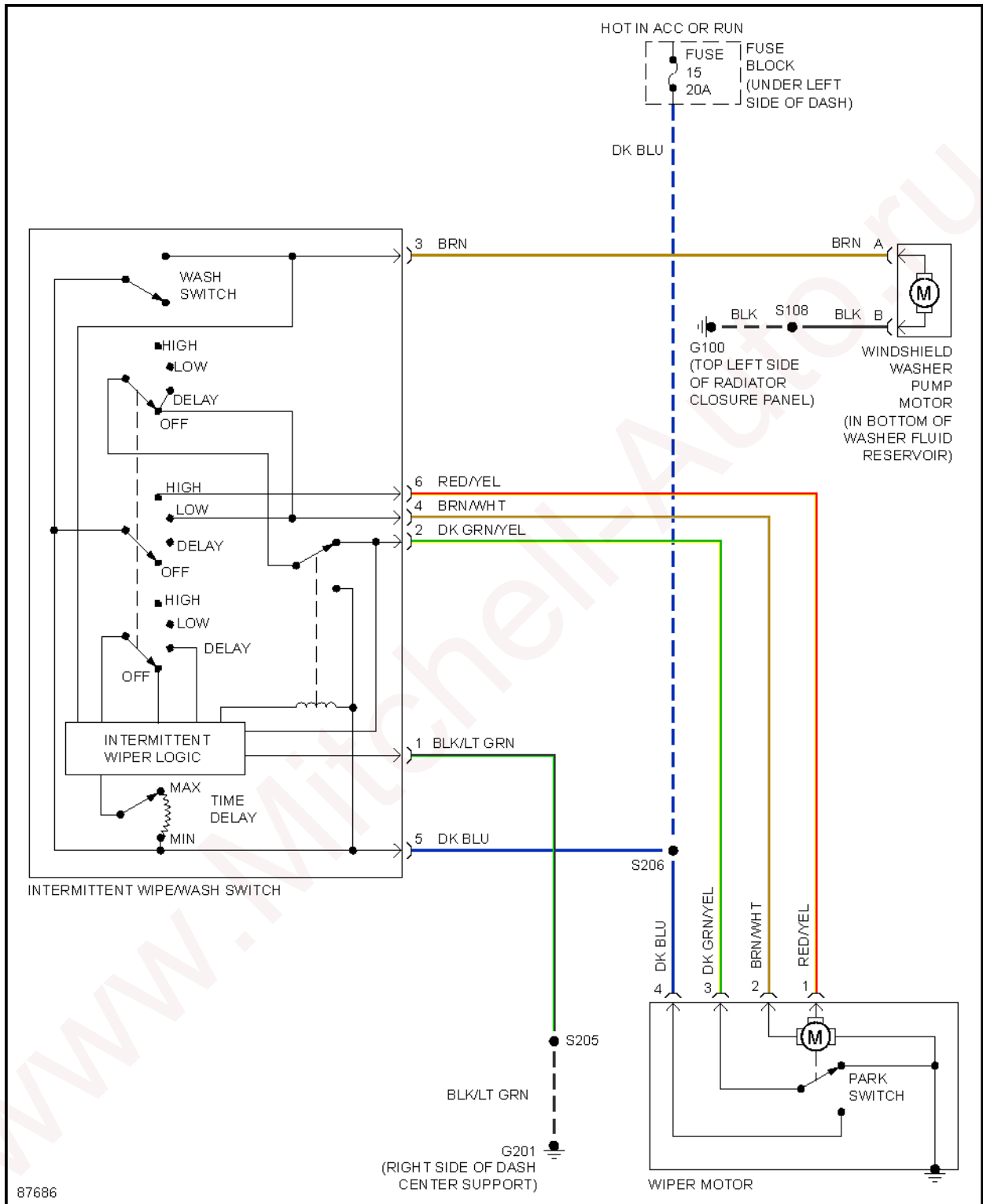


Fig. 36: Interval Wiper/Washer Circuit